

# Würth Electronics (UK) Ltd



## Practical EMI Filter Design Considerations – Part 1

19th September 2017

Presented by

**Mohamed AlAlami**  
Field Application Engineer - UK

# Agenda

- **Magnetics and Materials**
- **EMI Transmission Modes and Filter Topologies**
- **REDEXPERT**
- **Practical EMI Filter Design Considerations**



# MAGNETICS AND MATERIALS

# What is an Inductor ?

... technical aspect

- a piece of wire wrapped on something

We also see inductance ...

- as parasitic effects
- What are the main difference between these inductors?

THE INDUCTOR IS USED  
TO STORE THE ENERGY

■ **DC/DC converter topology**

- Buck
- Boost
- Sepic






# Inductors/Ferrites

- **Shape & size : Different construction**
  - THT, or SMT
  - Toroidal , Solenoidal (Rod core), Multilayer
  - Shielded or not shielded
  - Wire (Round, Flat, Multi-wire,..)
  
- **Different material**
  - NiZn
  - MnZn
  - Iron alloy
    - Superflux
    - WE-Perm
    - WE-Perm2
  - Iron Powder



# Core Material - Permeability

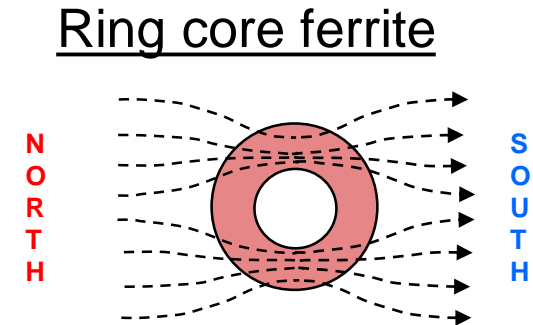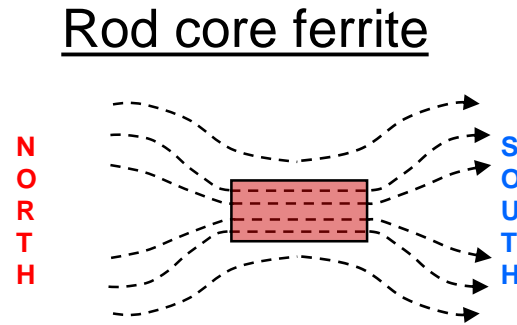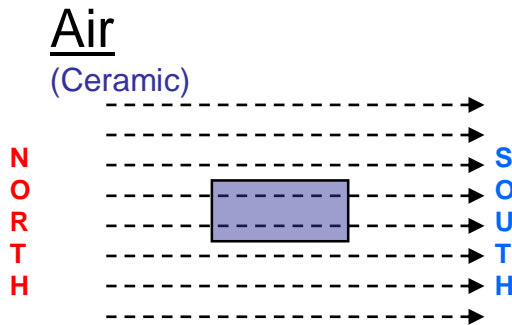

Induction in air:

$$B = \mu_0 \cdot H$$

linear function, because  $\mu_r = 1 = \text{constant!}$

Induction in a ferrite:

$$B = \mu_0 \cdot \mu_r \cdot H$$

material-  
frequency-  
temperature-  
current-  
Pressure-

  
DC Bias Current

Demo

The relative permeability is a:

-dependent parameter

# Core Material - Permeability


## Relative permeability

- describes the capacity of concentration of the magnetic flux in the material

$$\mu_r = \frac{1}{\mu_0} \frac{\Delta B}{\Delta H}$$

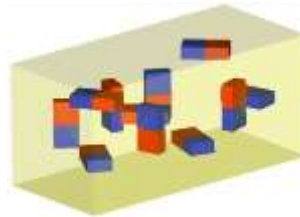
## Ferrite material

- unordered (random position)
- soft magnetic



## Permanent magnet

- ordered
- hard magnetic

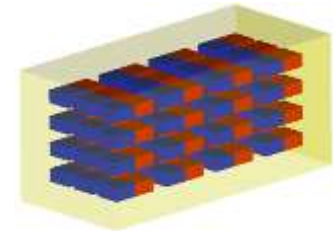

## Typical permeability $\mu_r$ :


- Iron Powder/ Superflux: 50 ~ 150
- Nickel Zinc (NiZn): 40 ~ 1500
- Manganese Zinc (MnZn): 300 ~ 20000

# Core Material – Permeability




=1 turn

NiZn  
MnZn  
Iron Powder

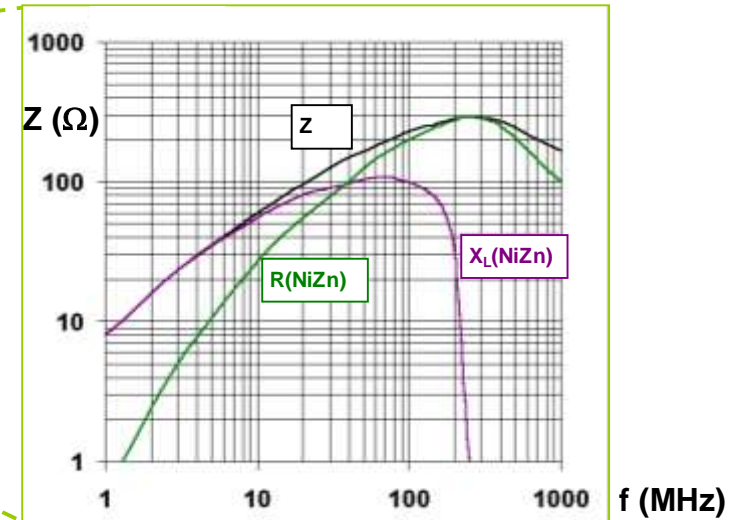

Core material-Parameter

Replacement circuit

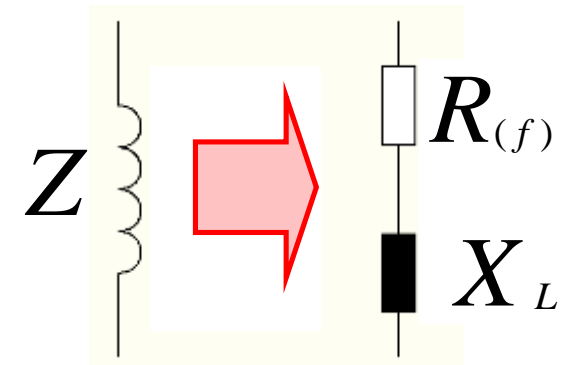


$$Z = \sqrt{R_{(f)}^2 + X_L^2}$$


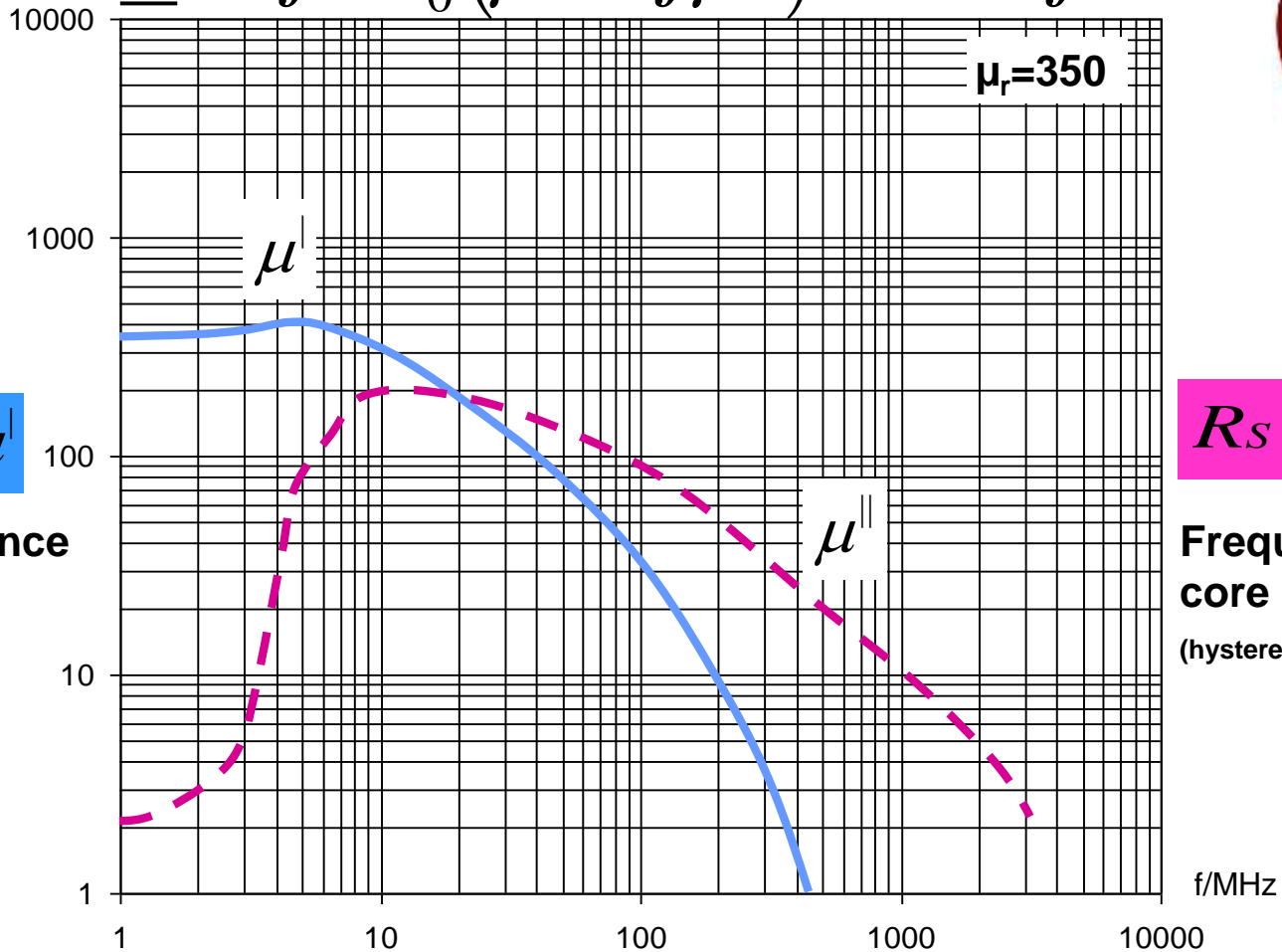
# Core Material – Permeability

$$\underline{Z} = j\omega L_0 (\mu' - j\mu'') = R + jX$$




$$X_{LS} = \omega L_0 \mu'$$

**Inductive reactance**  
(Magnetize ability)


$$R_s = \omega L_0 \mu''$$

**Frequency dependent core losses**  
(hysteresis loss)

# Core Material – Resistance

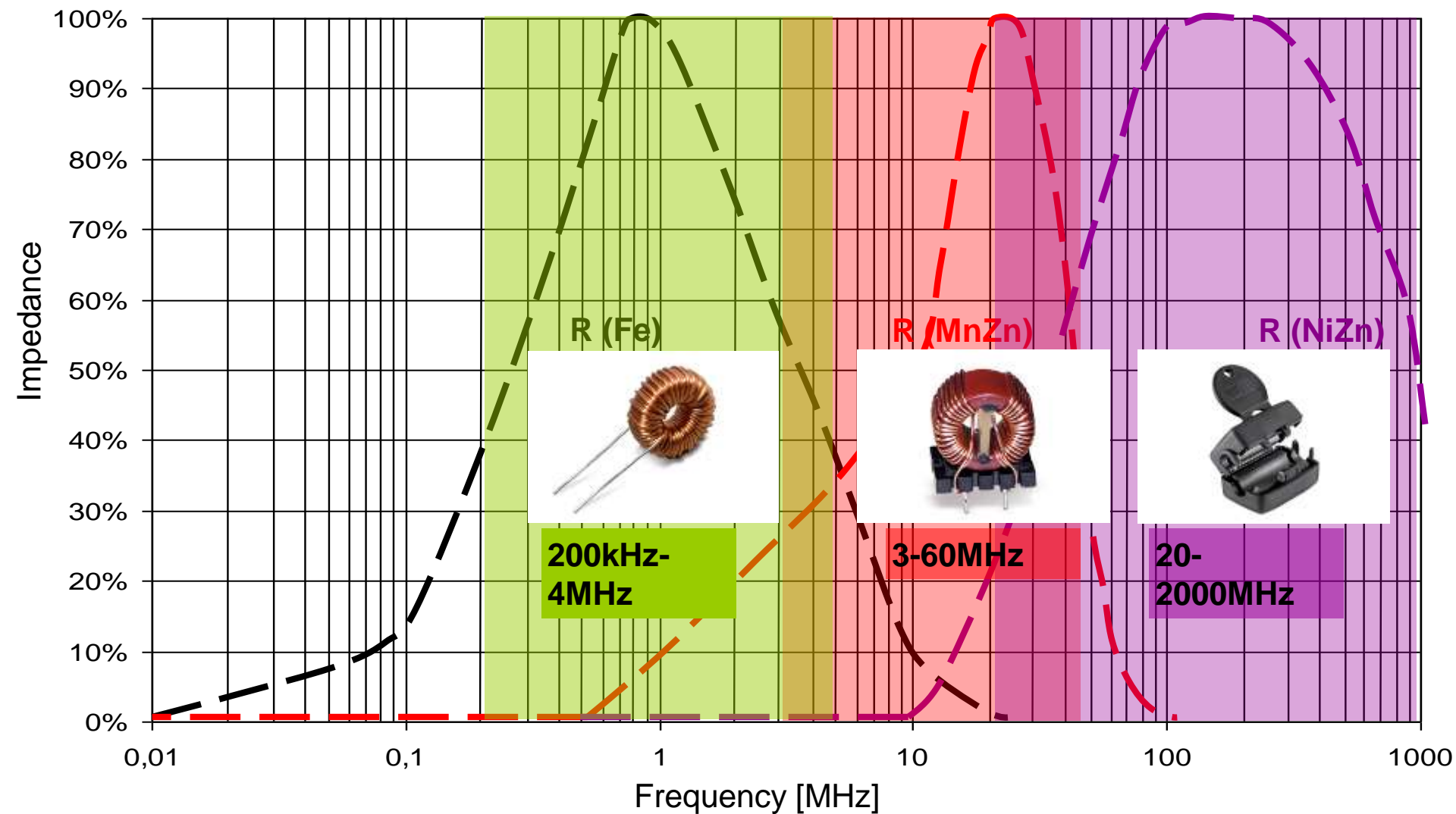

# Core Material – Inductance

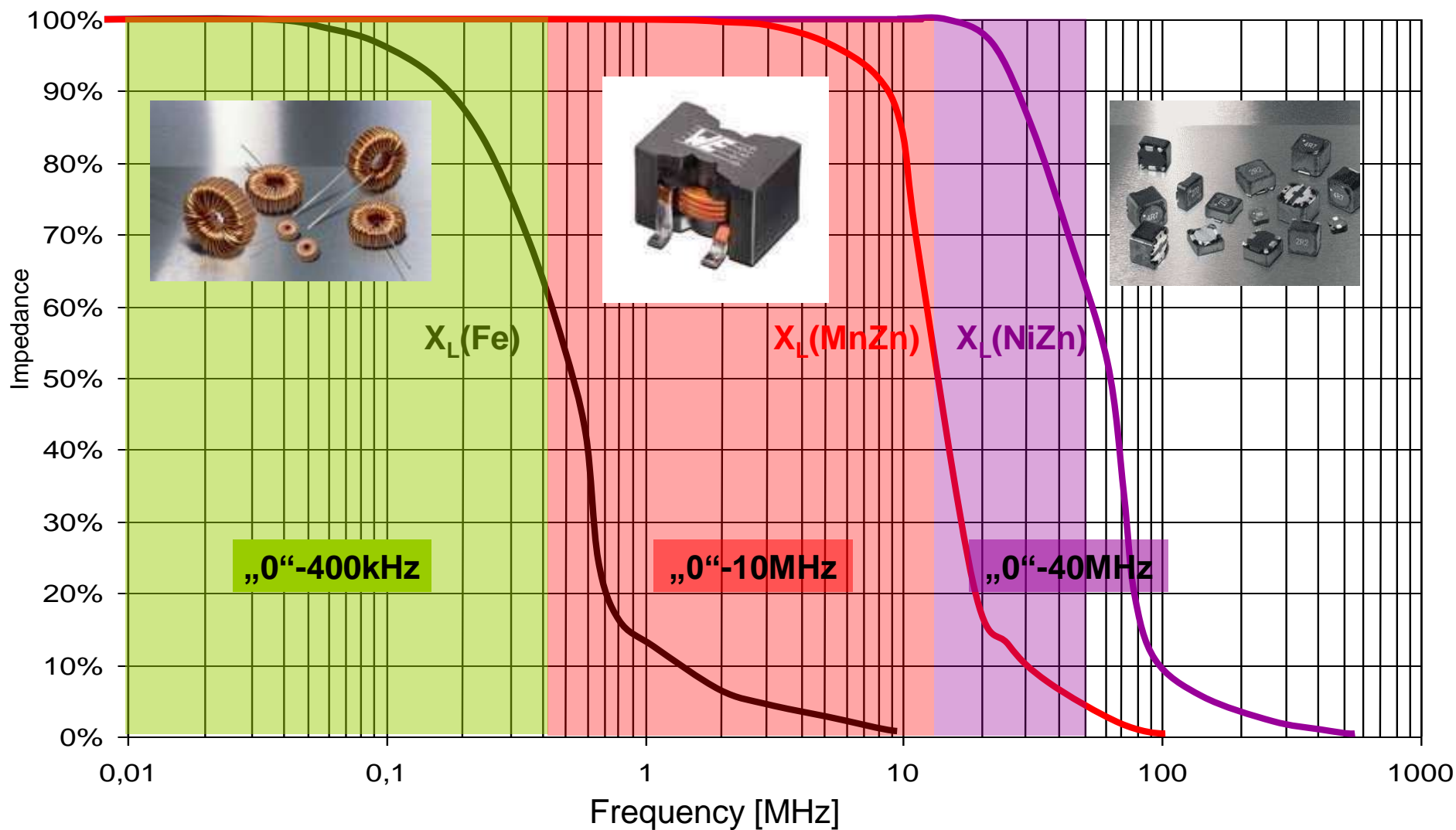

# Core Material – Saturation/Frequency


Core Materials	Core Loss	Perm f(DC bias)	Relative Cost	Frequency Range	Saturation Flux density ( $B_{sat}$ )	Temp Stability
Iron Powder	Highest	-	Lowest	200kHz	15.000 Gauss (1,5 Tesla)	-
Ni Zn	Lowest	-	Low	10MHz	4.500 Gauss (0,45 Tesla)	-
WePerm	Low	++	Low	3 MHz	10.000 Gauss (1.0 Tesla)	++
SuperFlux	Medium	+++	Medium	1.0 MHz	12.000 Gauss (1,2 Tesla)	+++

**Switching Frequency ⇔ Core Material**
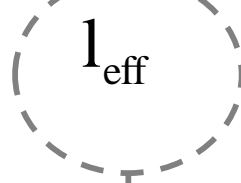
# INDUCTOR / inductance



$$L = \frac{(\mu_0 * \mu_r * A_{eff} * N^2)}{l_{eff}}$$



$$l'_{eff} \sim l_{eff} + l_{gap} \mu_r$$



Higher  $l_{eff}$




Lower L



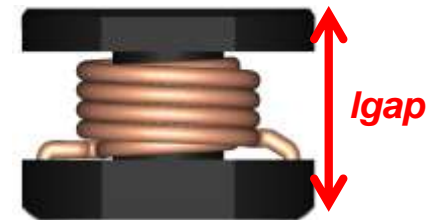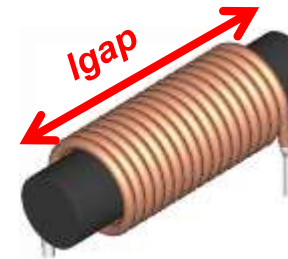$\mu_r$  = relative permeability  
 $N$  = No. of turns  
 $A_{eff}$  = effective magnetic area  
 $l_{eff}$  = effective magnetic length



# Core Material – Shielding

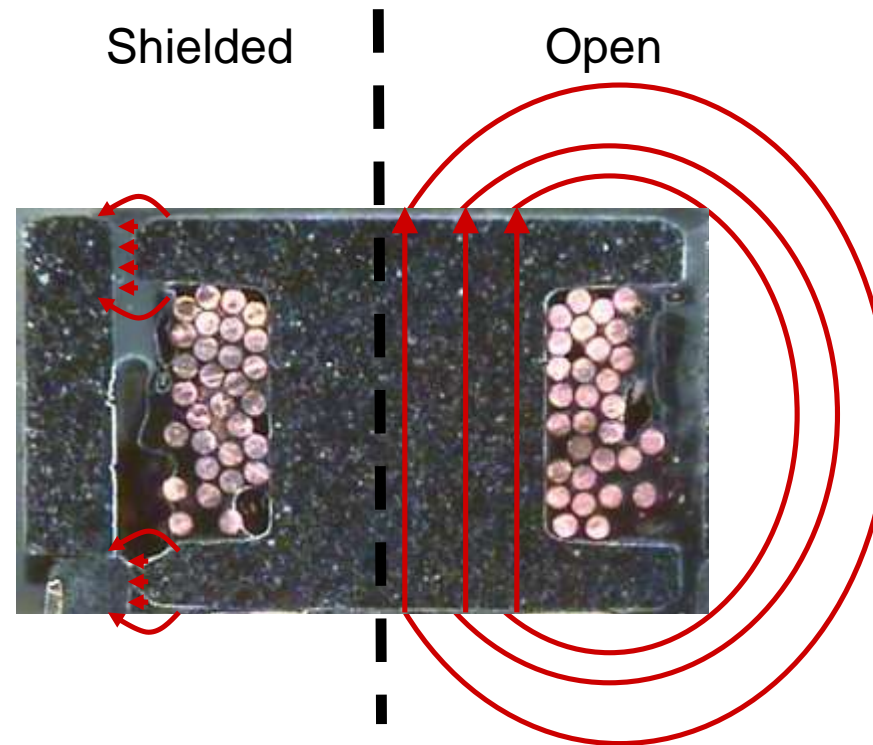

Advantage of the shielded inductor => smaller Gap

⇒ Less turns to reach the L value => Lower DCR compare to a open version


⇒ With big air gap the inductance is less dependent of the core material

# EMI TRANSMISSION MODES AND FILTER TOPOLOGIES

# EMC Impact
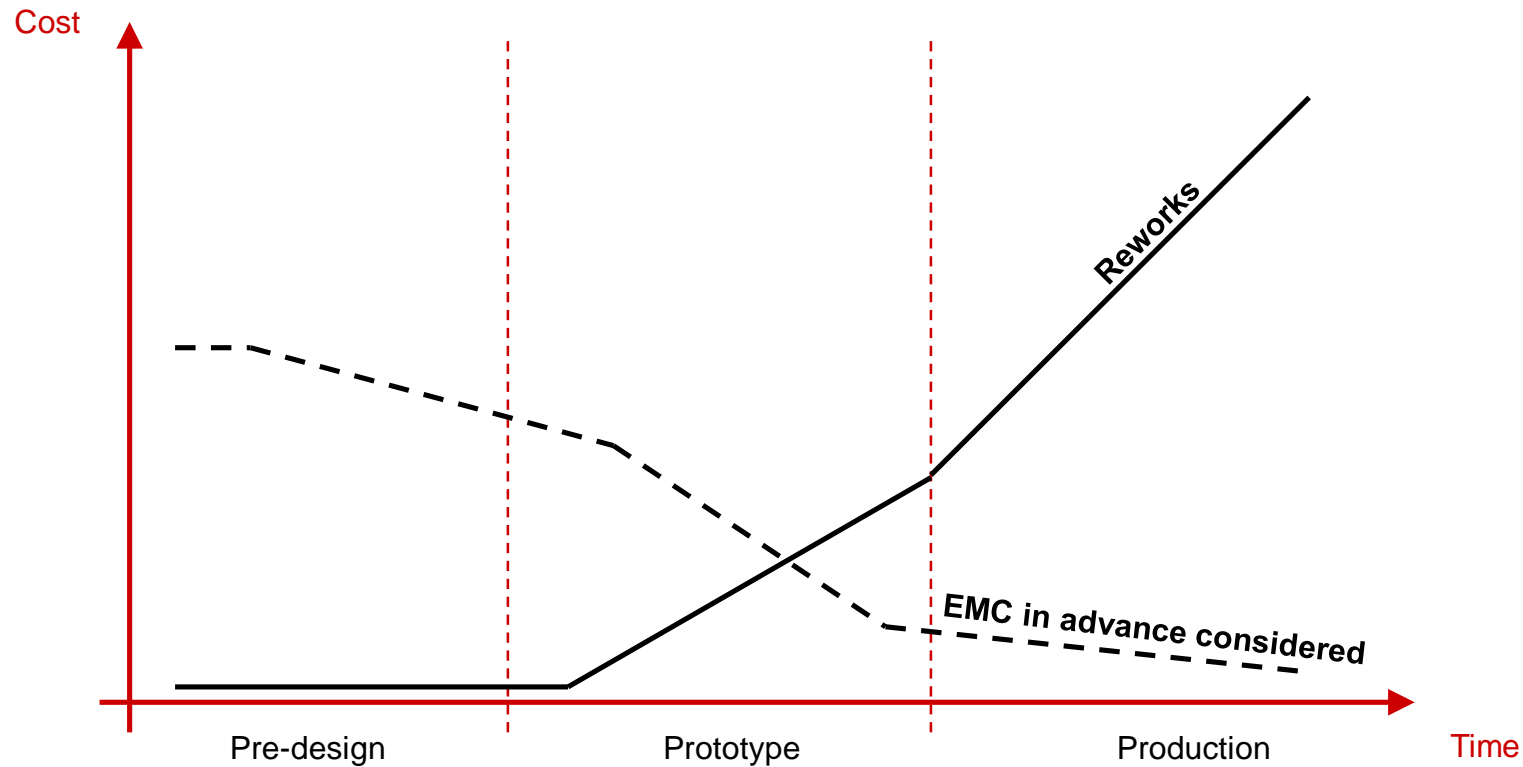
## Economical point of view:

- Dependent on when EMC conformity is considered in a design phase





# What causes EMI in a product?



- **Clock frequencies.** E.g Crystal 25MHz,  
CPU 2.6GHz



- **Data rates.** E.g USB 2.0 480Mbps,  
SATA II 300Mbps



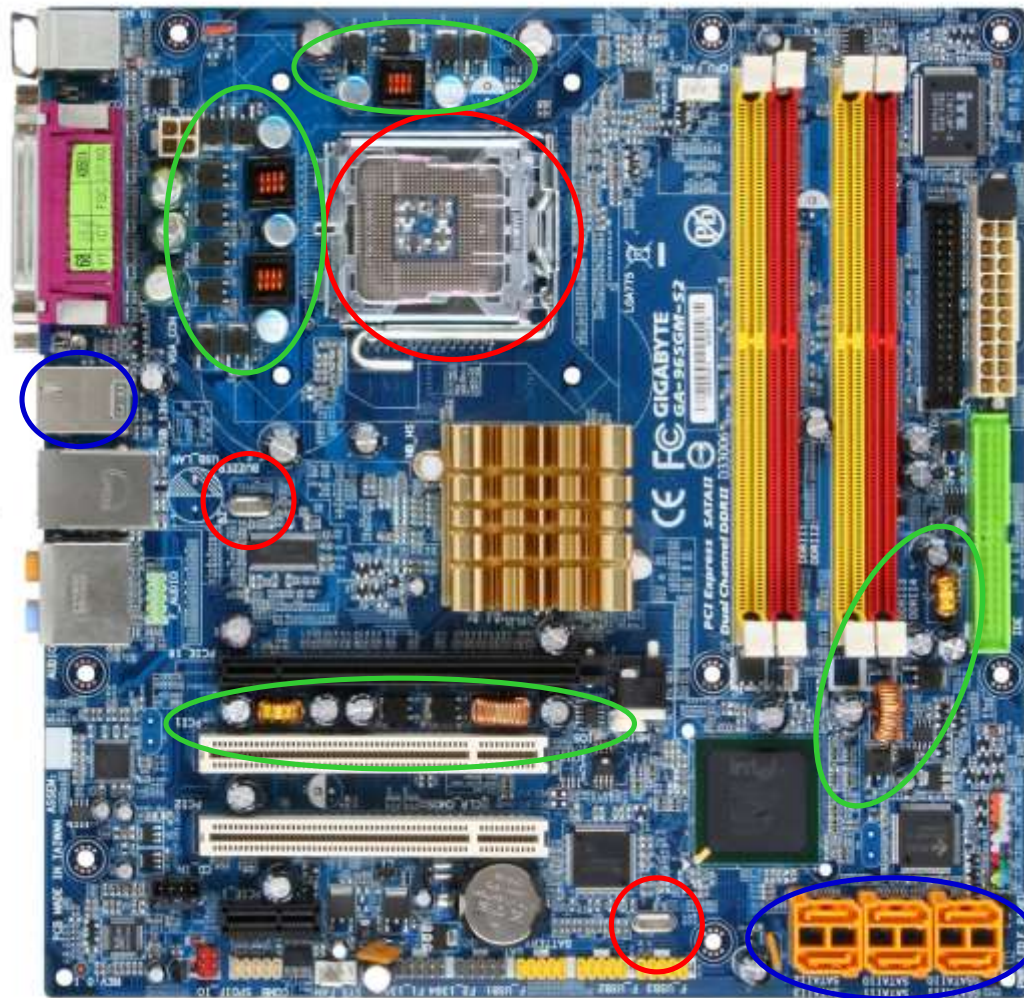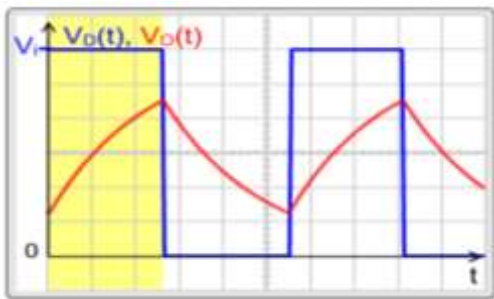- **DC/DC convertors and Switch mode power supplies (SMPS)** E.g 135kHz, 2MHz



# Transmission modes


- Recognize the transmission mode:

## Differential Mode (DM)

Signals on a  
line(s) with a return path
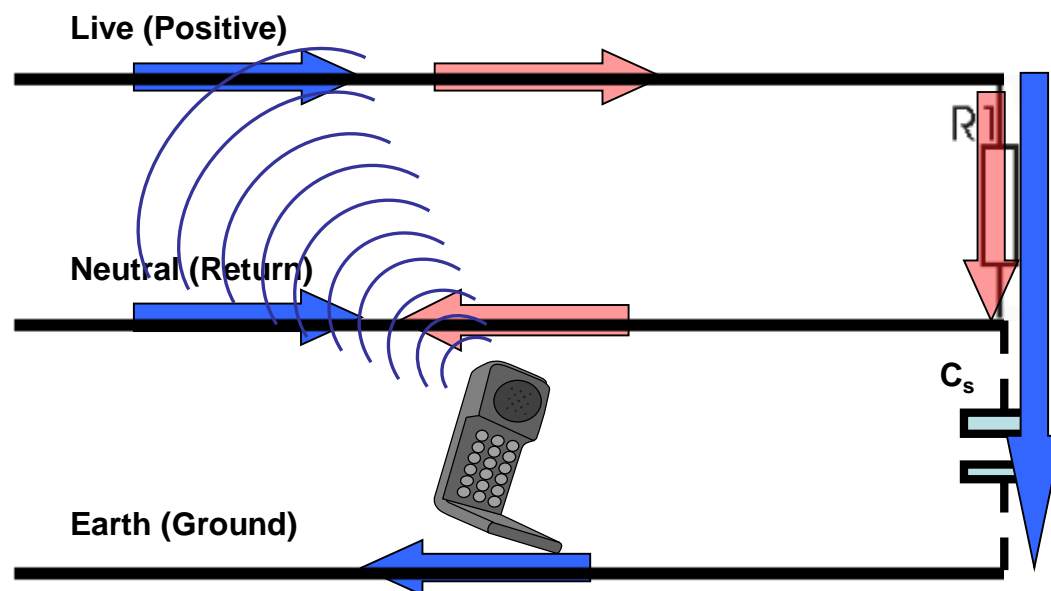
## Common Mode (CM)

Noise on all lines  
propagating in the  
same direction with  
respect to earth



# EMC – Coupling

## → Primary procedure


...to aim to source a low noise

## → Secondary procedure


... eliminate the noise through interrupting the coupling way

## → Tertiary procedure

... increase the noise immunity at load

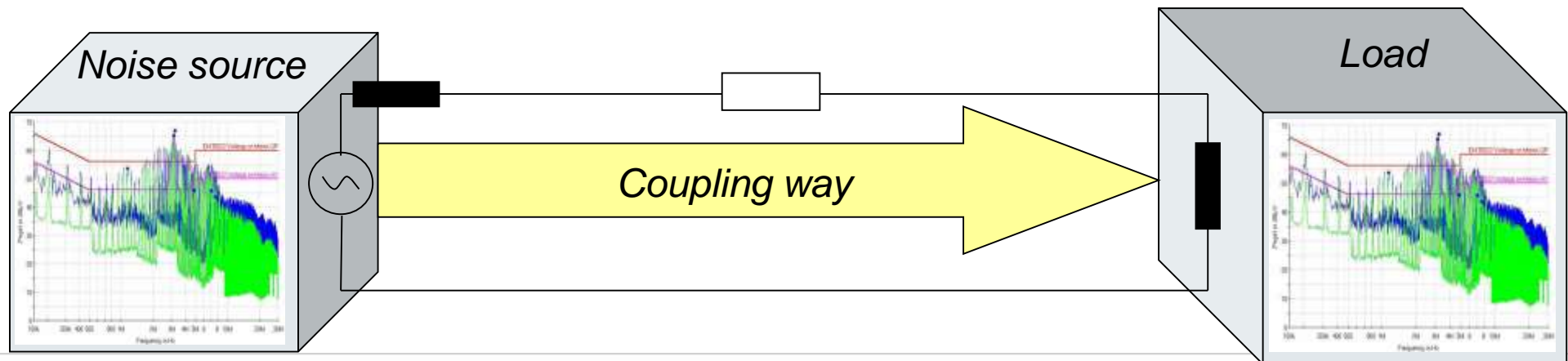
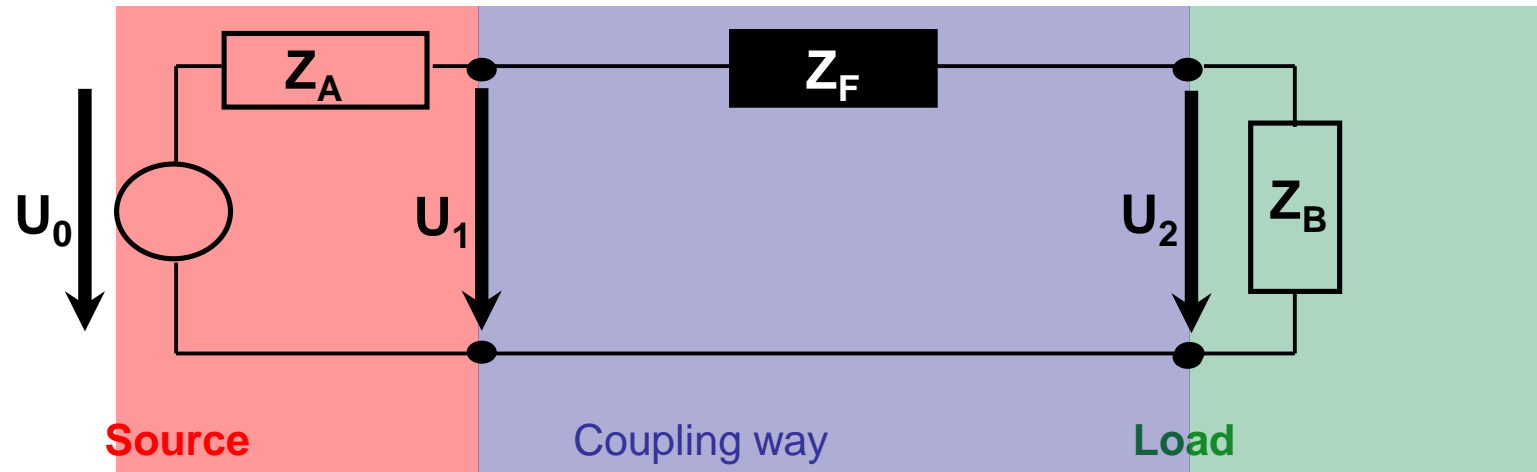
# Insertion loss – Mathematical Definition



- System attenuation

$$A = 20 \cdot \log \frac{Z_A + Z_F + Z_B}{Z_A + Z_B} \quad \text{in (dB)}$$

- Impedance

$$Z_F = \left[ 10^{\frac{A}{20}} \cdot (Z_A + Z_B) \right] - (Z_A + Z_B) \quad \text{in } (\Omega)$$

# Insertion loss – Differential Filter Topologies

## Source Impedance





low

high

high or  
unknown

low

low or  
unknown

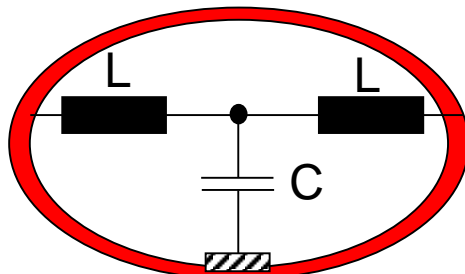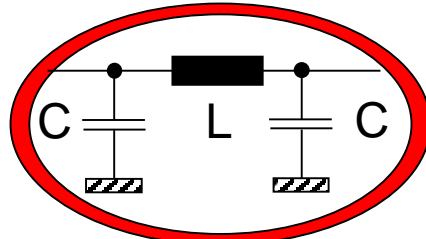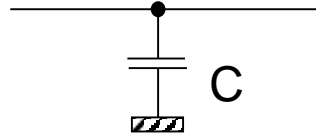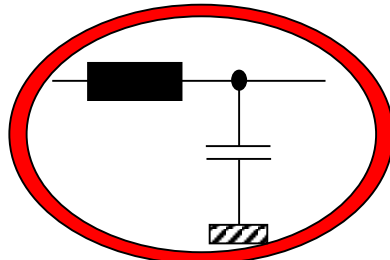

## Load Impedance

high

high

high or  
unknown

low

low or  
unknown

→ small C = higher SRF







Choose ferrite bead  
= build no resonance with C  
= broadband filter

Pay attention to:  
**SRF of used  
components**



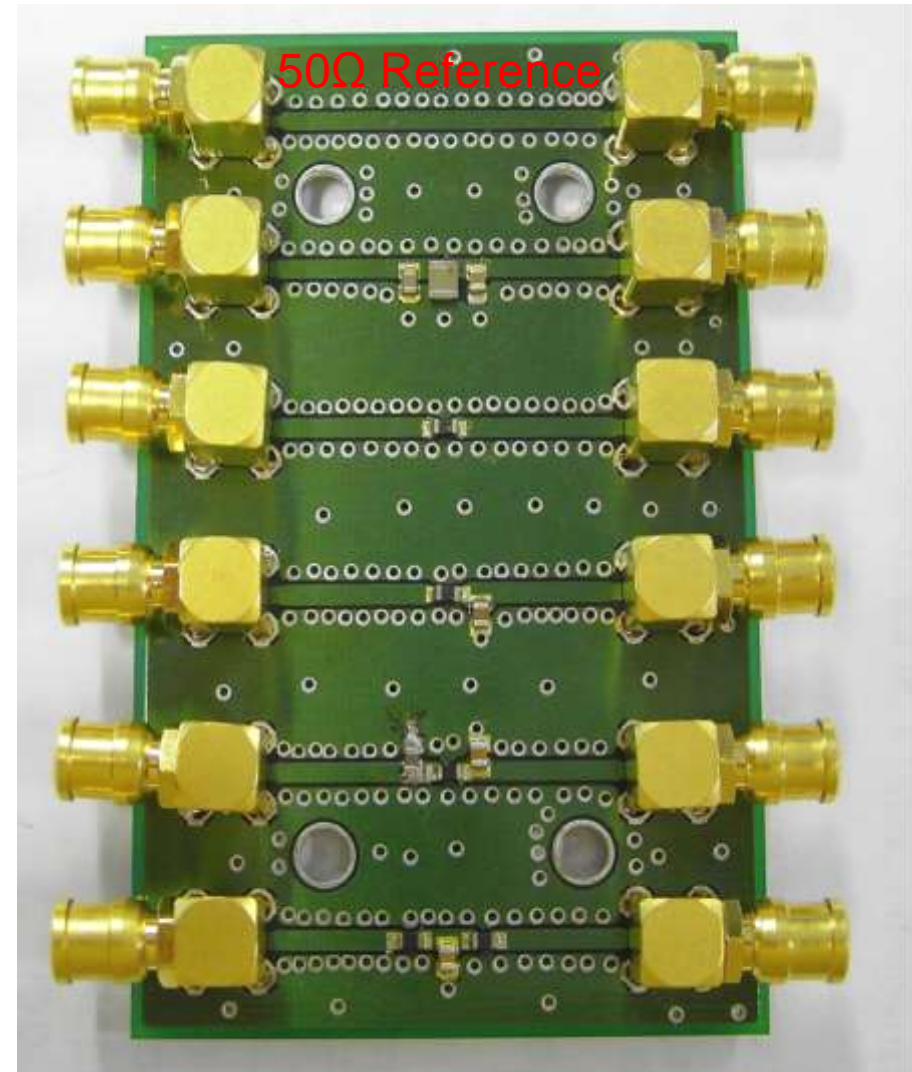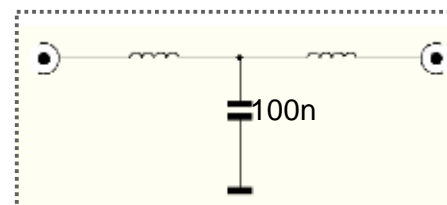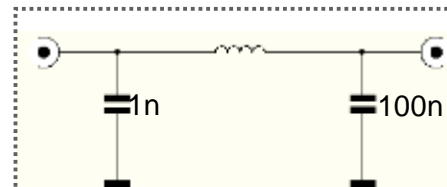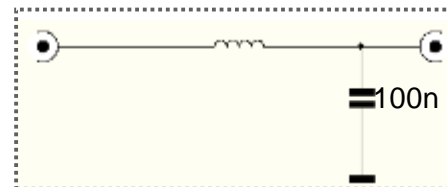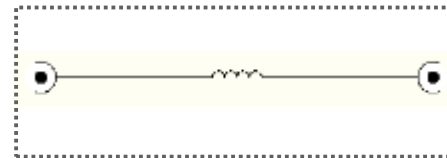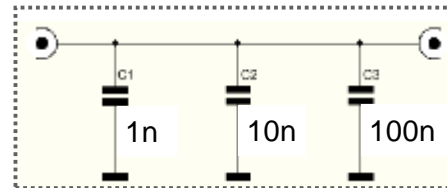
# Filter topologies – Demo board




- Parallel-C-filter
- L-filter
- LC-filter
- $\Pi$ -filter
- T-filter


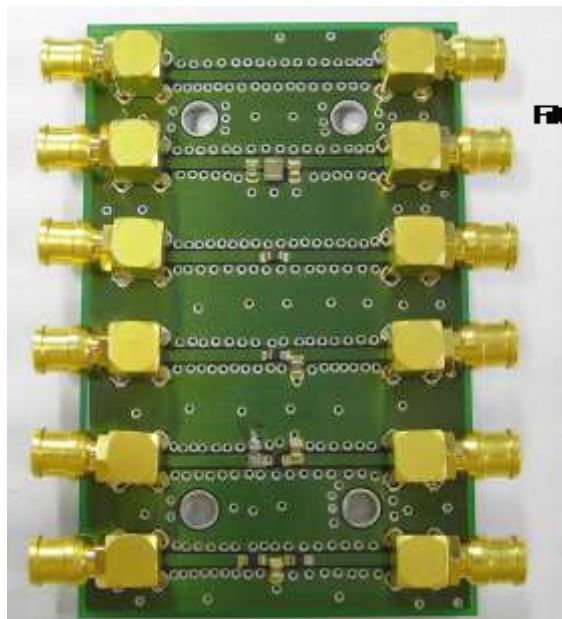
# Filter Topologies – LT Spice Simulation





 Filter Topologies

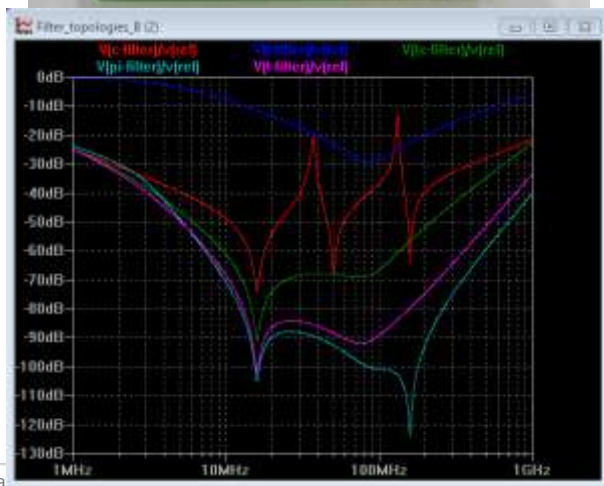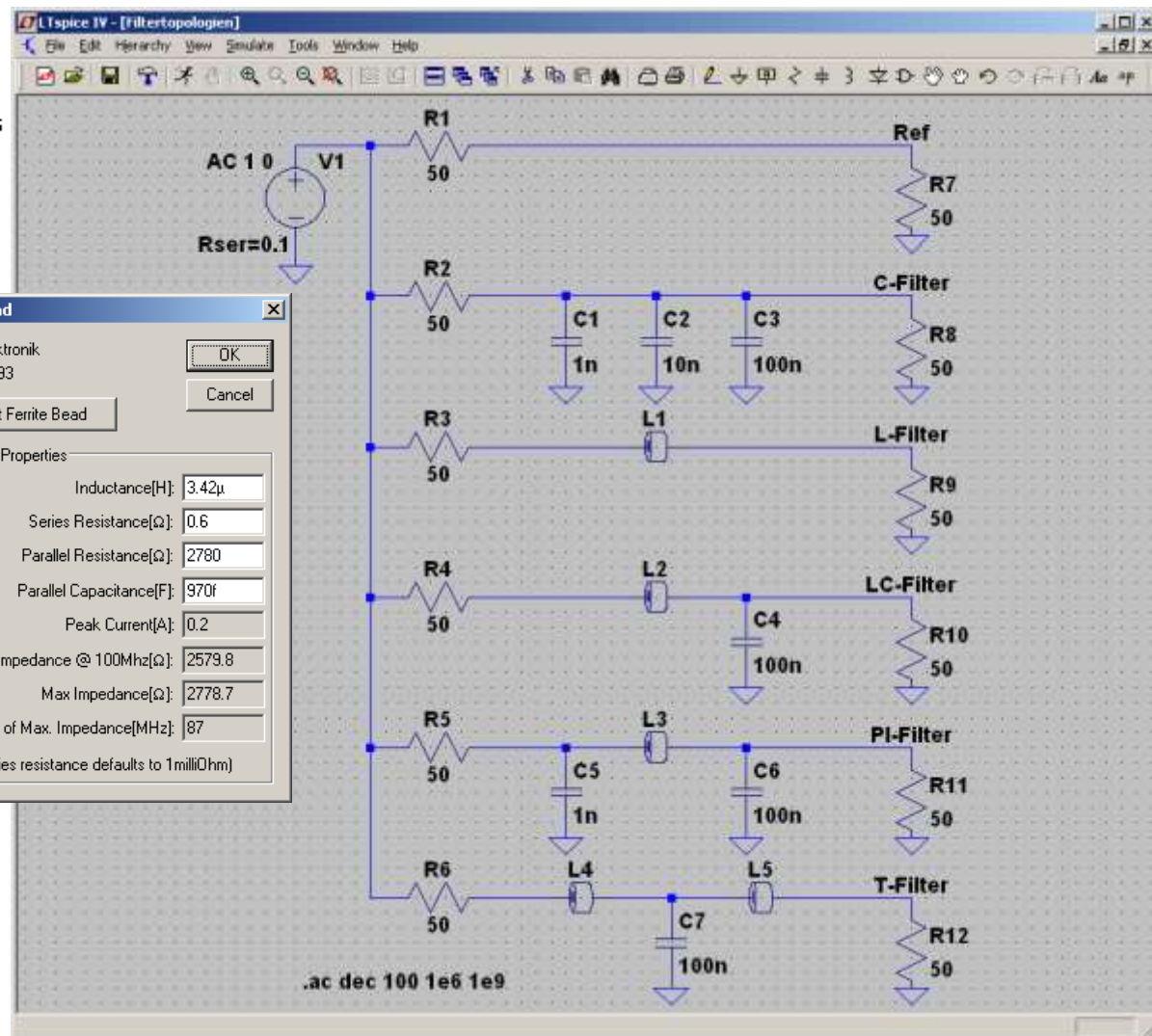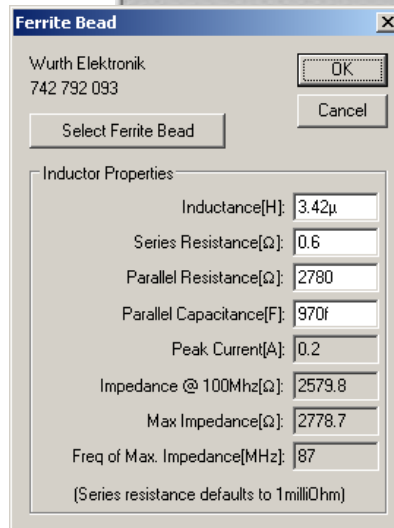

# Filter topologies – L-filter

- L-filter

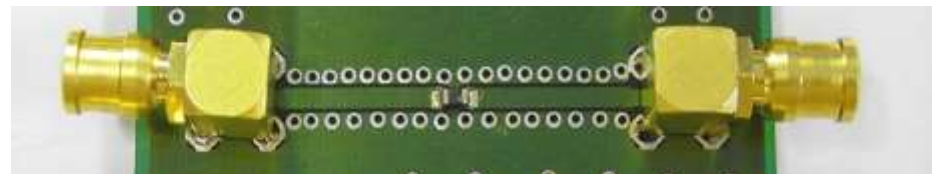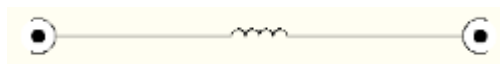

- A chip bead ferrite is used as an inductance.


- WE-CBF 742 792 093:

$$Z_{\max} = 3000\Omega @ 80\text{MHz}$$

$$A = -29\text{dB} @ 80\text{MHz}$$

Simulated



Measured

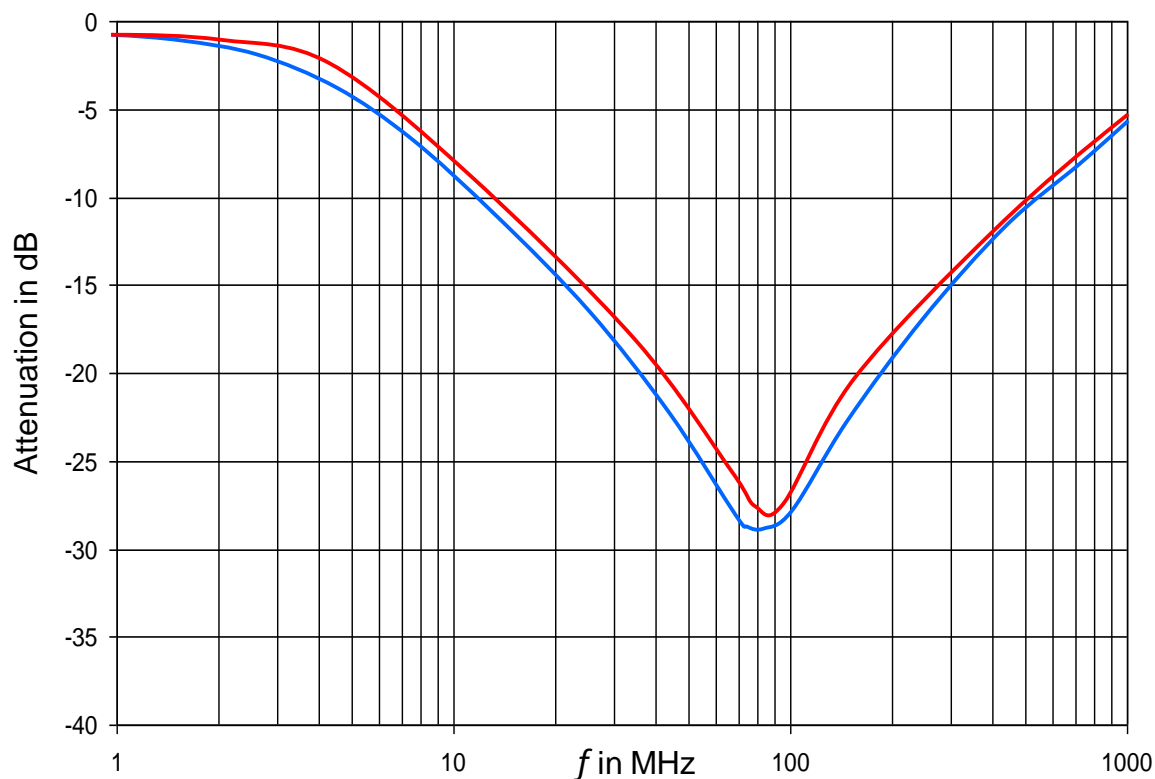



# Filter topologies – Parallel-C-filter

- Parallel-C-filter

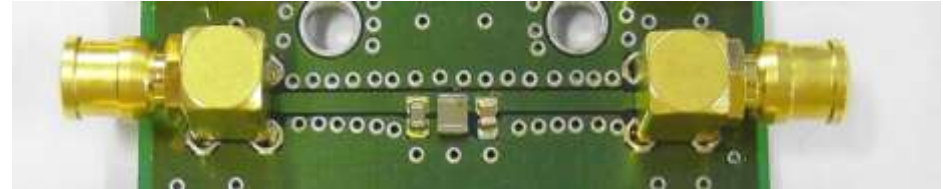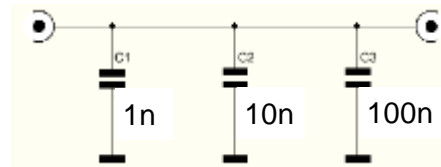


- Comparison of measurement and simulation

$$f_{\text{res}} = \frac{1}{2\pi \cdot \sqrt{L_s \cdot C}}$$

Example:



$$L_s = 1\text{nH}$$

$$f_{\text{res,C3}} = 15.915\text{MHz}$$

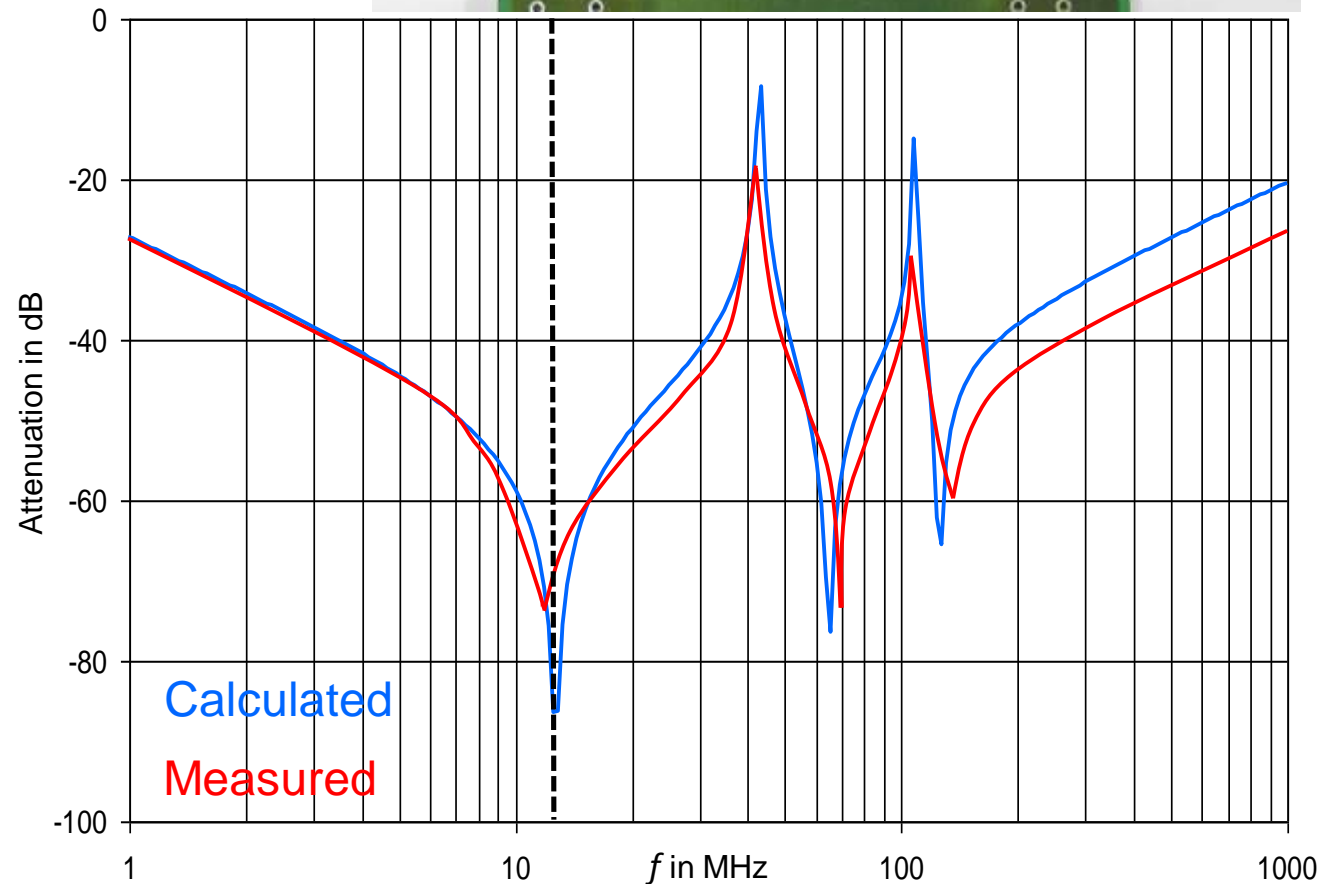

# Filter topologies – LC-filter

- LC-filter

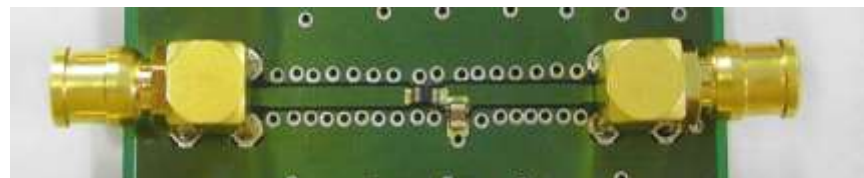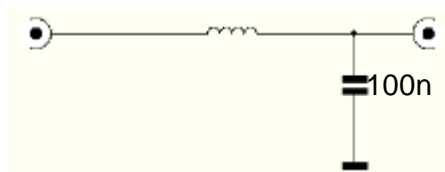


- Comparison of measurement and simulation

WE-CBF 742 792 093

$C = 100\text{nF}$



Simulated

Measured

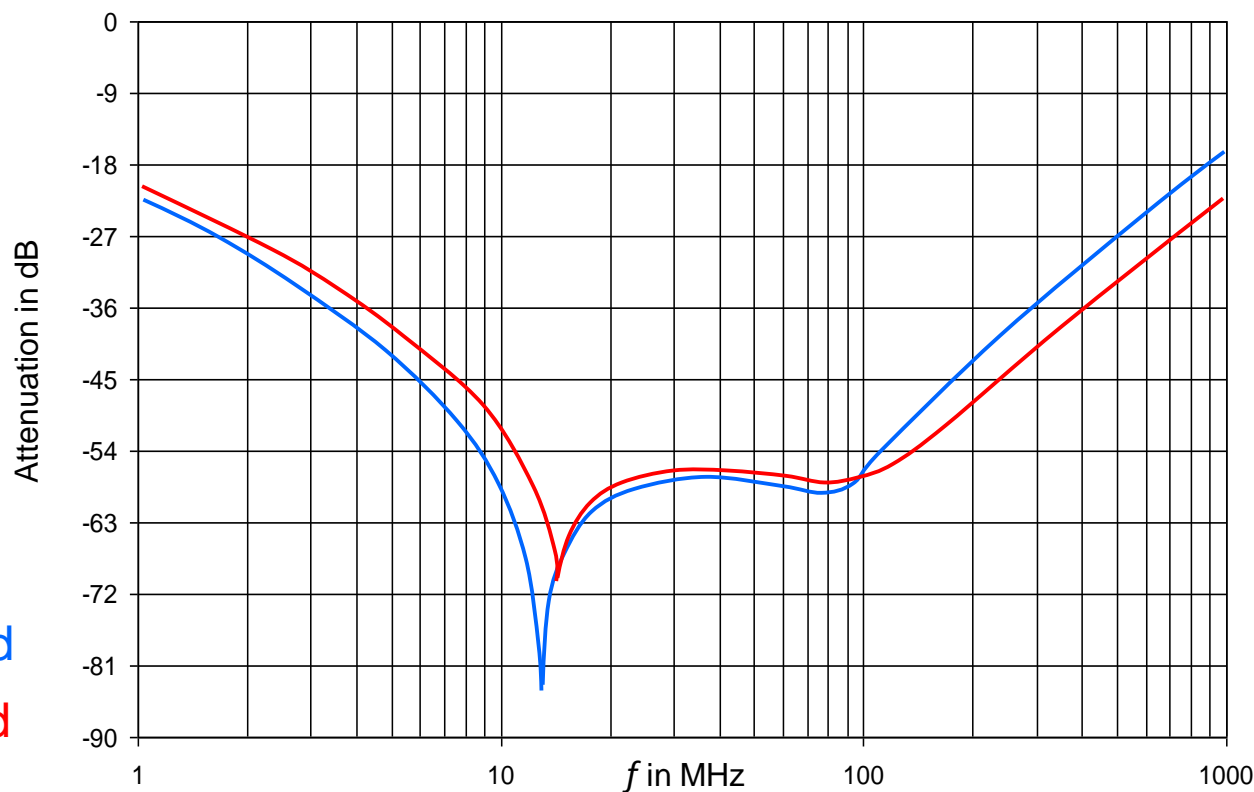

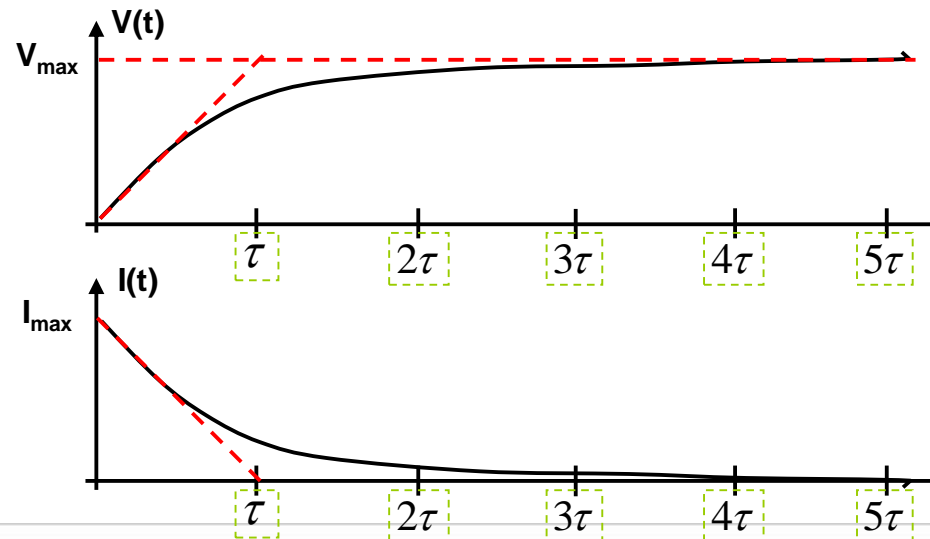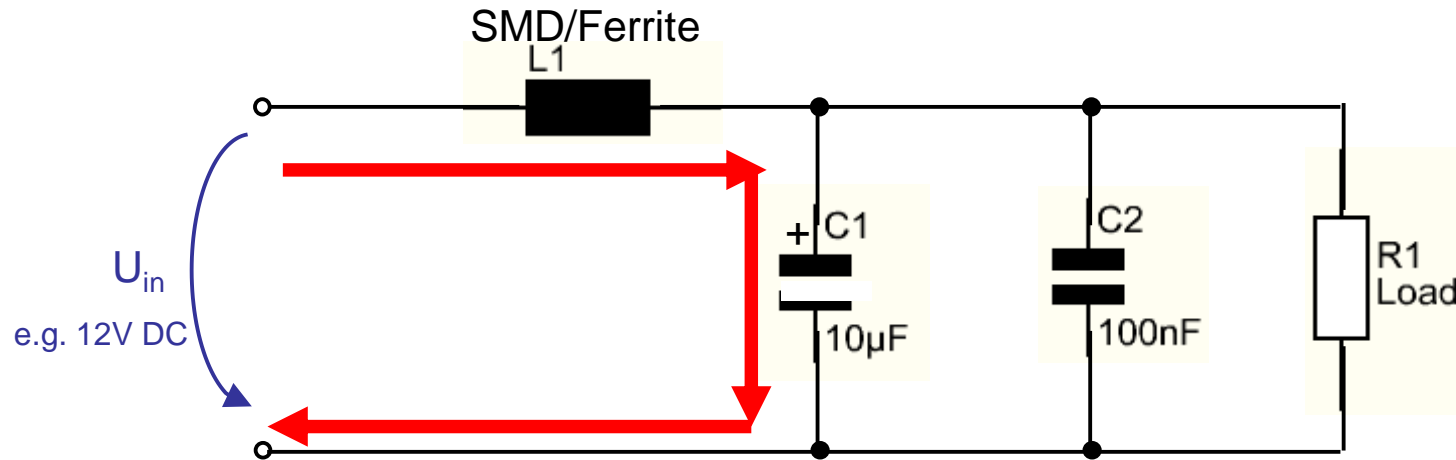
# Filter topologies – LC-filter

Avoiding inrush current damage to SMD ferrite beads



# Filter topologies – LC-filter

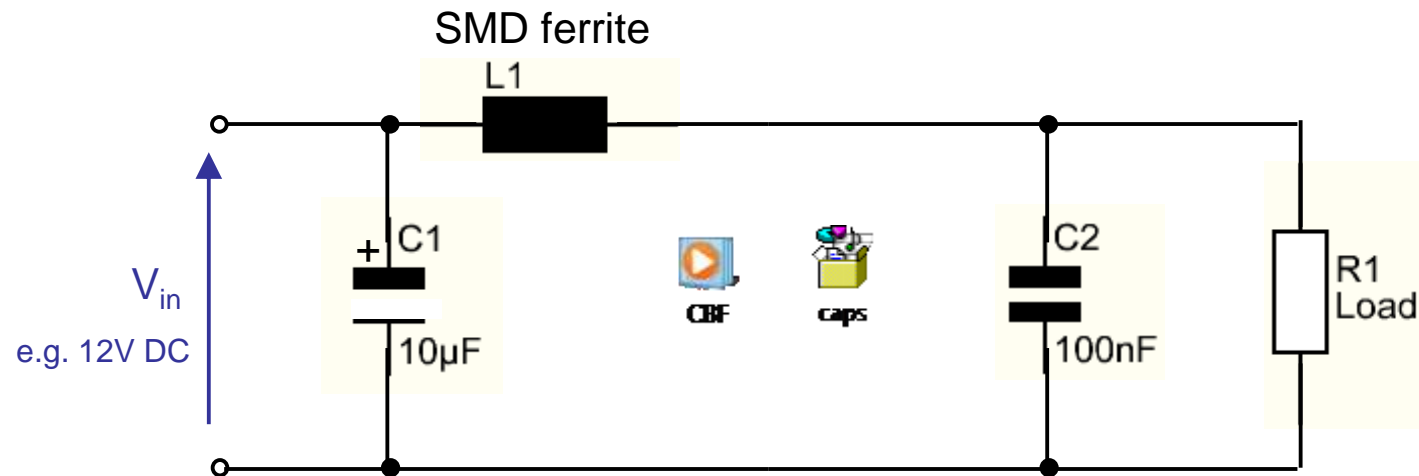
## Avoiding inrush current damage to SMD ferrite beads – Option 1



- Safety for SMD ferrite against inrush/pulse current
- Not a PI-Filter

# Filter topologies – LC-filter

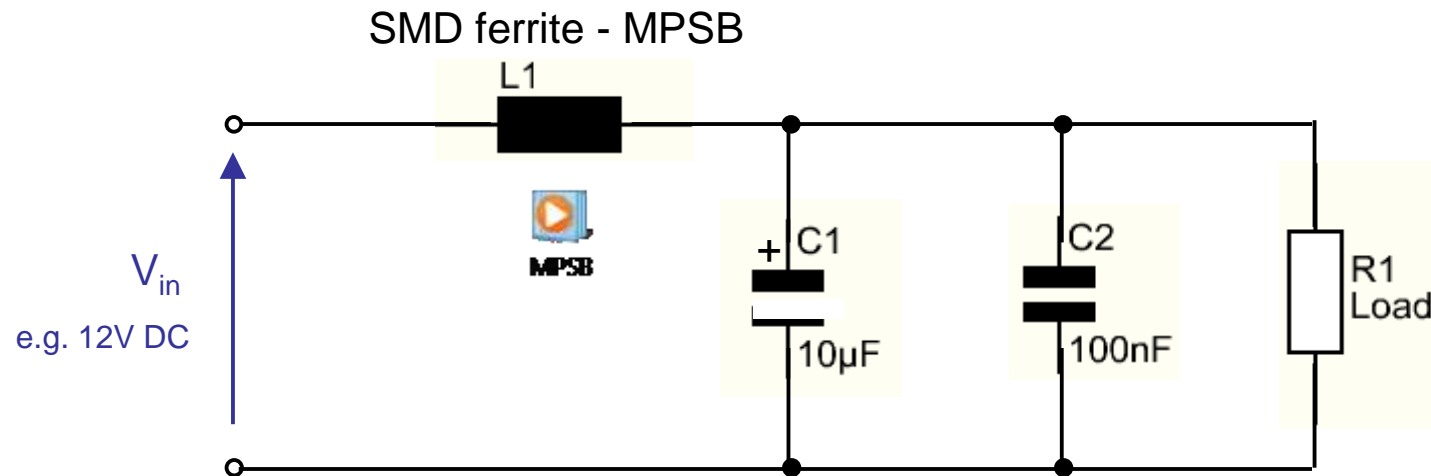
## Avoiding inrush current damage to SMD ferrite beads – Option 2



- Use inrush current (pulse) rated SMD ferrite (**WE-MPSB**)
- Preferred solution as:
  - High impedance termination

# Filter topologies – $\pi$ -filter

- $\pi$ -filter

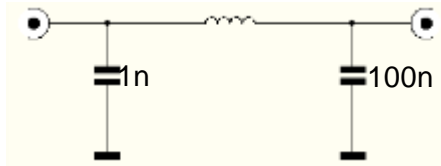

- Comparison of measurement and simulation


WE-CBF 742 792 093

$$C_1 = 1\text{nF}$$

$$C_2 = 100\text{nF}$$



Simulated

Measured

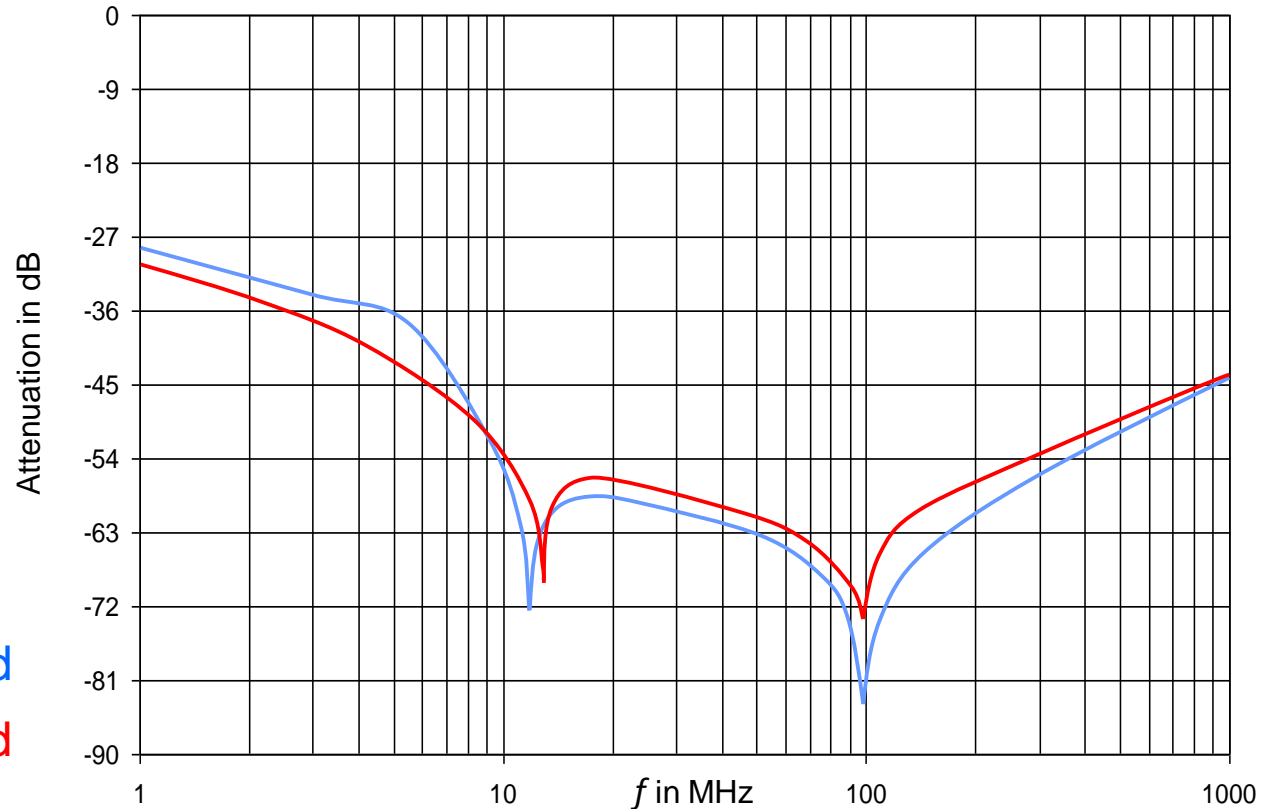

# Filter topologies – T-filter

- T-filter

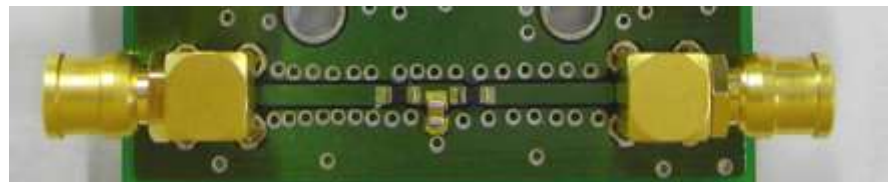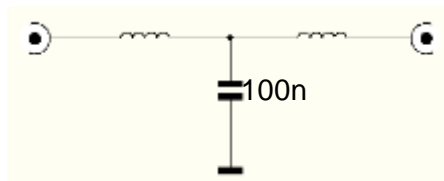

- Comparison of measurement and simulation


WE-CBF 742 792 040

WE-CBF 742 792 093

$C = 100\text{nF}$


Simulated

Measured

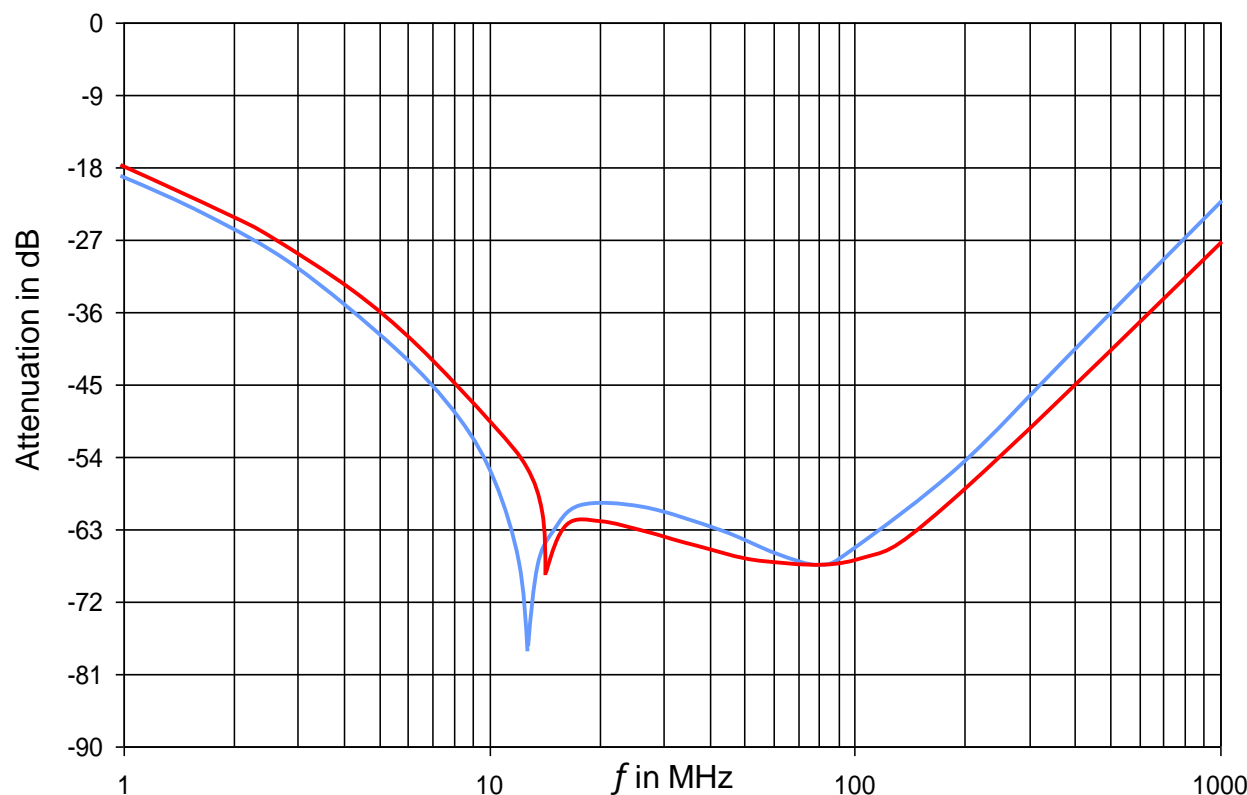

# Common Mode – Signal propagation

## Noise mode:

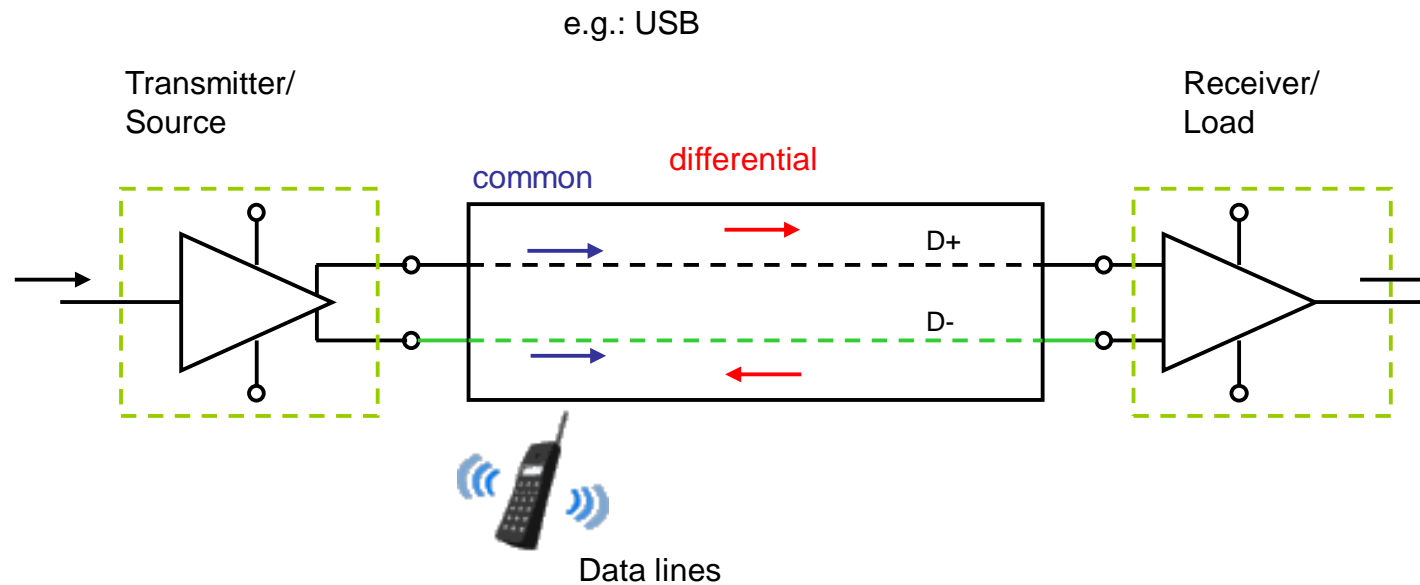

- Common mode noise
- Differential mode noise




# Common Mode Choke – Principle of Operation

It is a Bi-directional filter

- From device to outside environment
- From outside environment to inside device

Intended Signal - **Differential mode**

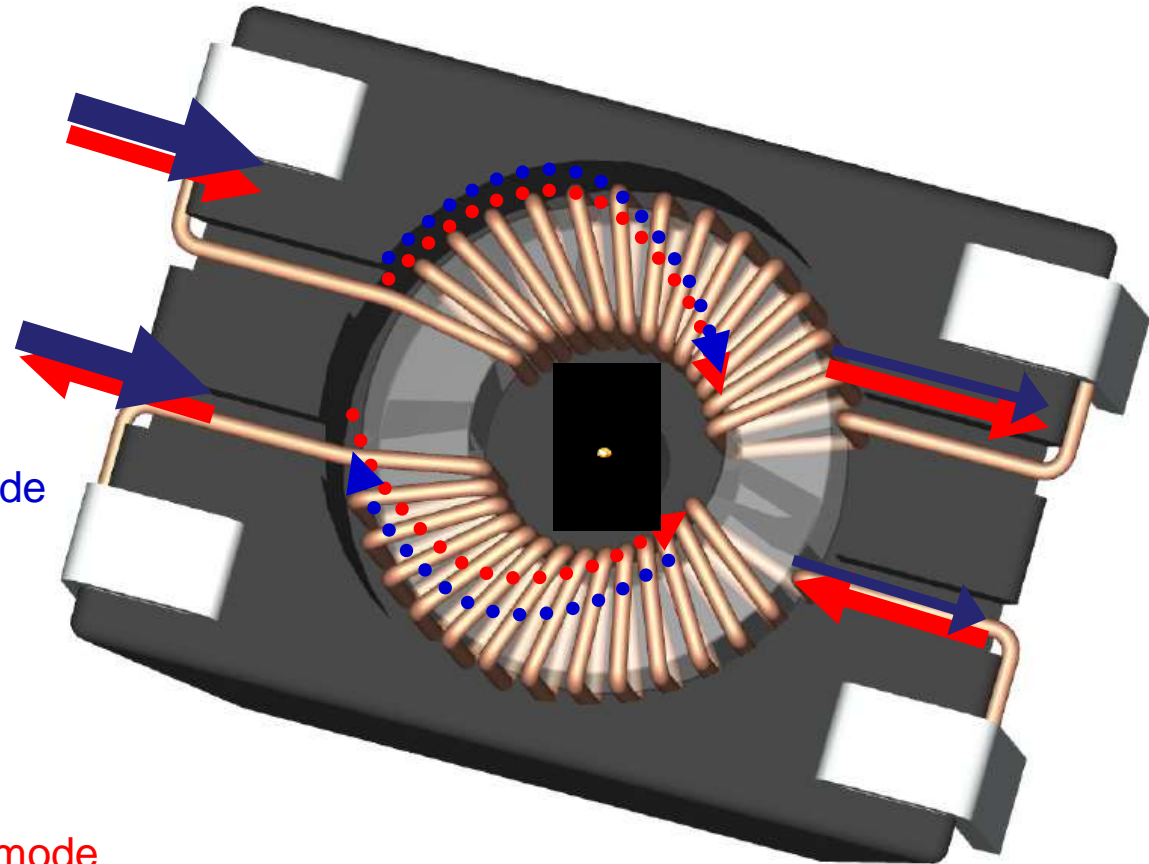Interference Signal (noise) – **Common Mode**




## Conclusion:

- “almost” no affect the signal - **Differential mode**
- high attenuation to the interference signal (noise) – **Common Mode**

# Common Mode Choke – Advantages


## Filter with two inductors

Filter input      Filter output

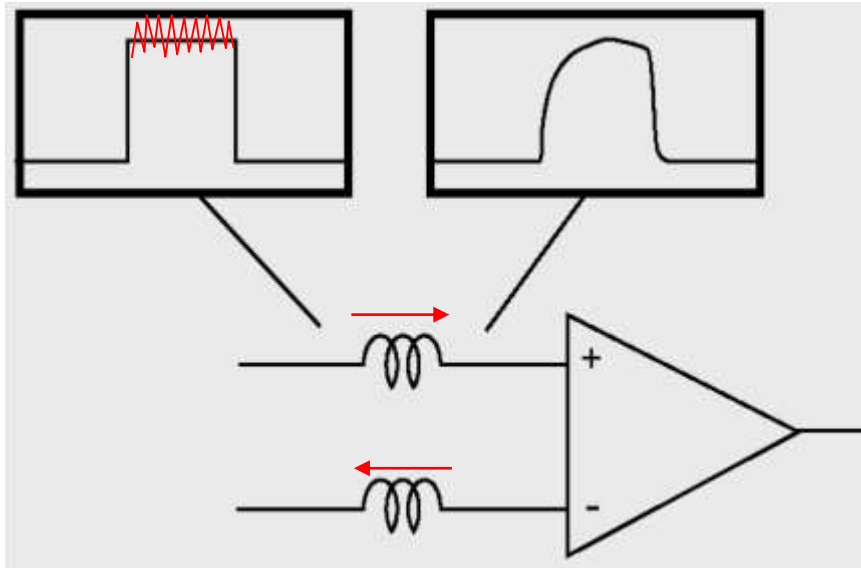


## Filter with CMC

Filter input      Filter output

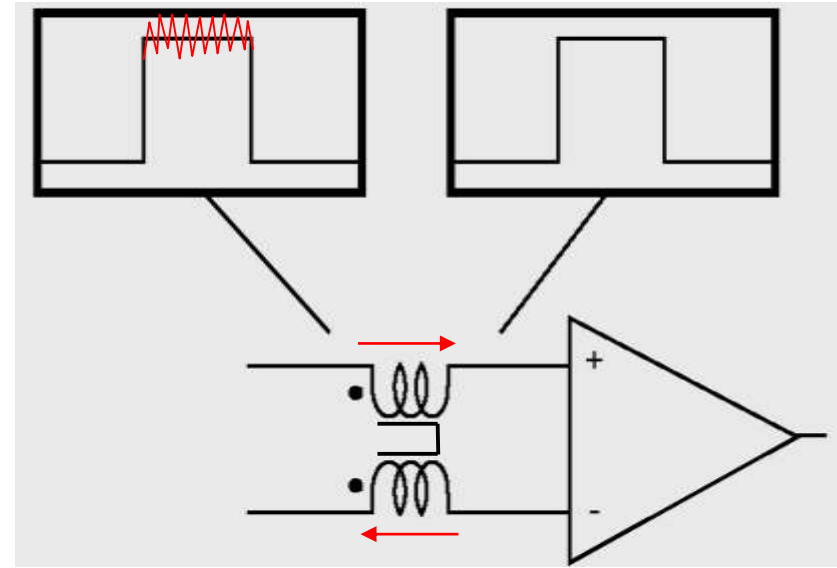


- Signal not affected
- Noise attenuated even close to the signal frequency

# Common Mode Choke – USB application



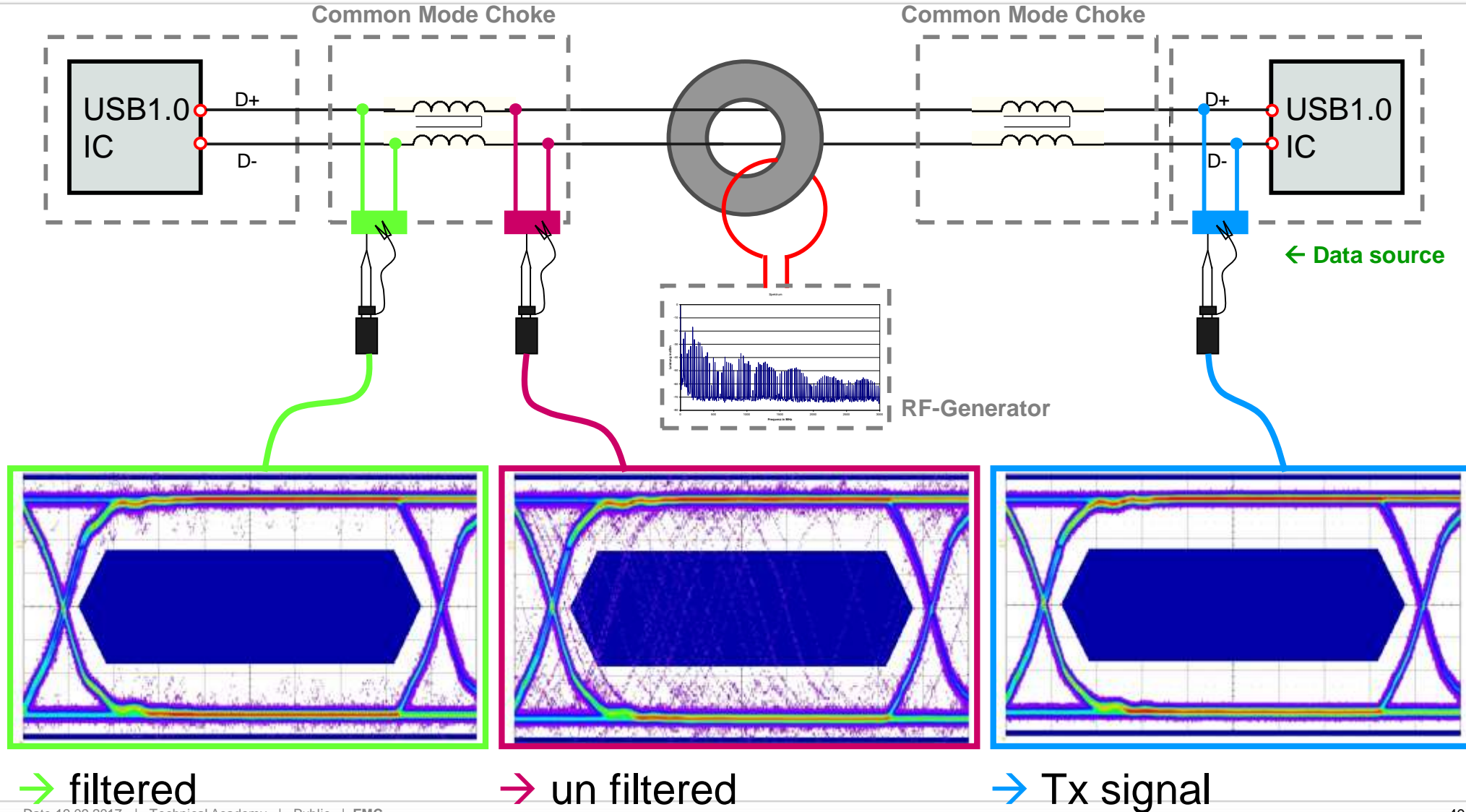


# Common Mode Choke – USB application

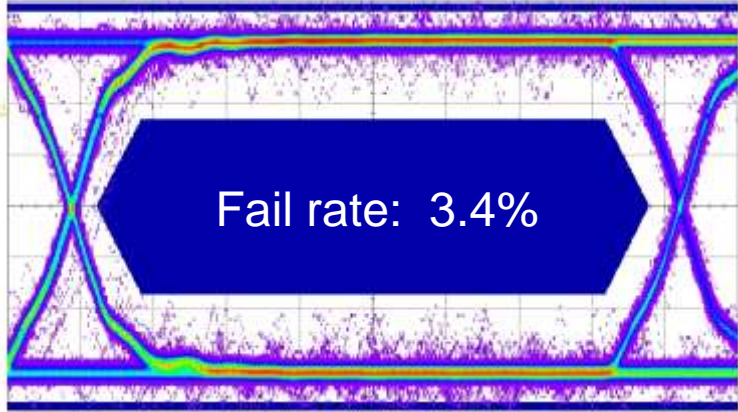

CM → 32 Ohm  
DM → 0.7 Ohm @ 12 MHz


CM → 363 Ohm  
DM → 1 Ohm @ 12 MHz

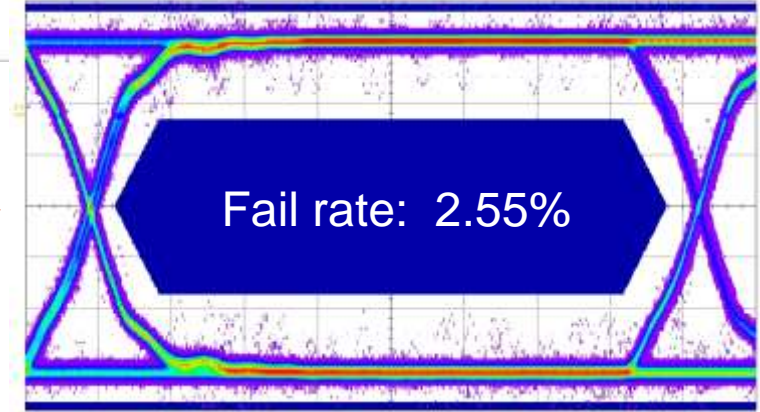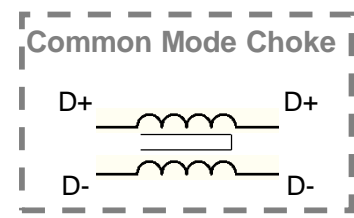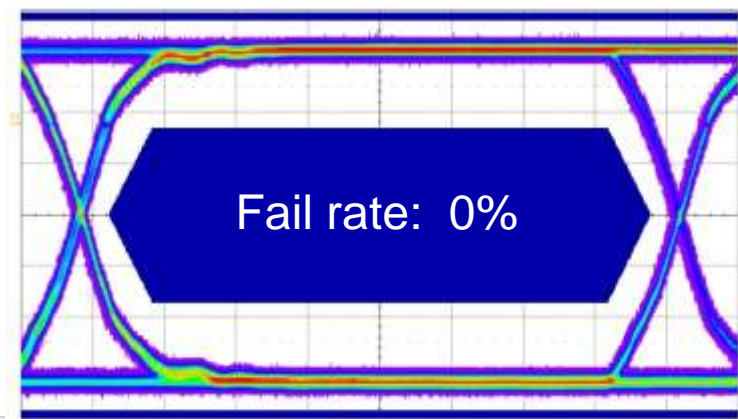

CM → 41 Ohm  
DM → 0.7 Ohm @ 12 MHz



CM → 77 Ohm  
DM → 1 Ohm @ 12 MHz

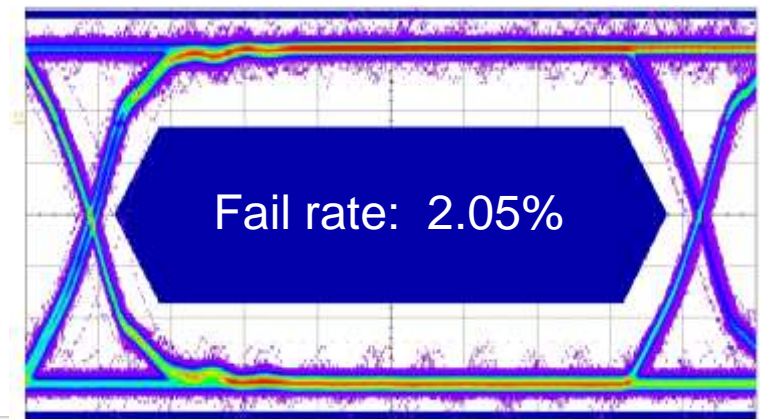



# REDEXPERT



# REDEXPERT



Power Inductors

**REDEXPERT**

## World's most accurate AC loss model

The losses determined with REDEXPERT are based on real time DCDC measurements with its typical current and voltage waveforms. Besides all core and winding losses they do also consider losses in the air gap.

▶ Calculate the AC losses



# User Interface



Würth Elektronik Group

Sign in

English ▾

more than you expect

## SELECTION TABLE

Power Inductors **REDEXPERT®** ▾

100 / 2082 items

✓	Series	Order Code	Spec	Type	L	R <sub>DC,typ</sub>	I <sub>R</sub>	I <sub>sat</sub>	Size	Length	Width	Height
✓	WE-MAPI	744383130068		Single	680 nH	101 mΩ	1.55 A	3.80 A	1610	1.6 mm	1.6 mm	0.90
✓	WE-MAPI	744383130082		Single	820 nH	115 mΩ	1.45 A	3.60 A	1610	1.6 mm	1.6 mm	0.90
✓	WE-MAPI	74438313010		Single	1.00 µH	127 mΩ	1.40 A	3.40 A	1610	1.6 mm	1.6 mm	0.90
✓	WE-MAPI	74438313012		Single	1.20 µH	140 mΩ	1.30 A	3.20 A	1610	1.6 mm	1.6 mm	0.90

## Design Tools

## STORAGE



744383130068

WE-MAPI · 1610  
680 nH · 101 mΩ  
1.55 A · 3.80 ADrop Order Codes  
in the bar to addDrag out buttons  
to delete them

Share

Free Samples

Tidy Up

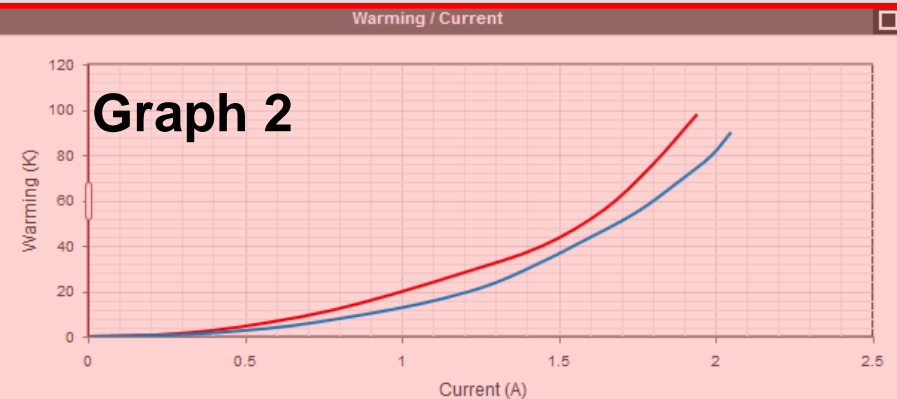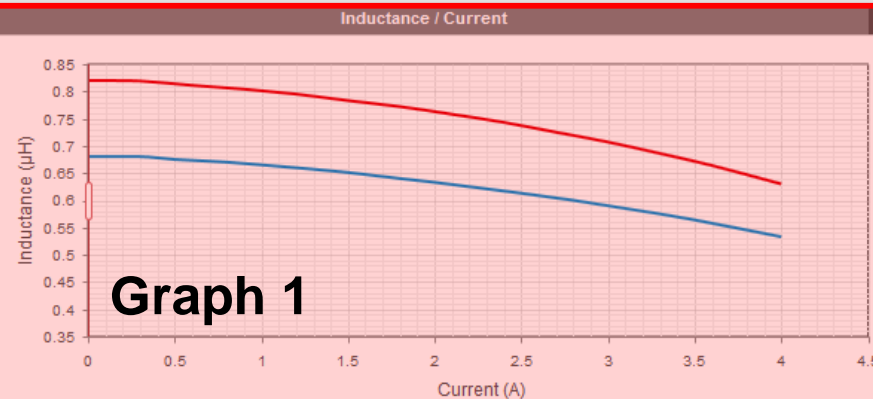

# REDEXPERT

<https://www.we-online.com/redexpert/#/module/1>



**[www.we-online.com/redexpert](https://www.we-online.com/redexpert)**



# PRACTICAL EMI FILTER DESIGN CONSIDERATIONS

# Common Mode Filter Design

## With Chassis / EMC Ground

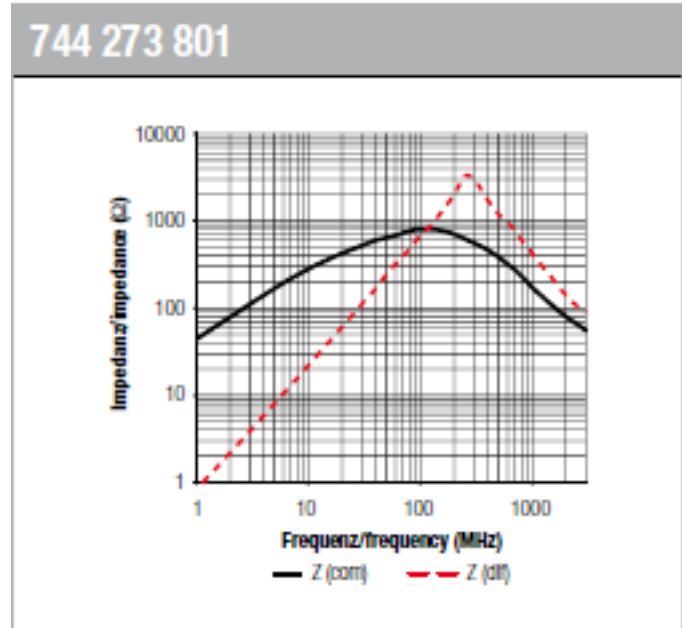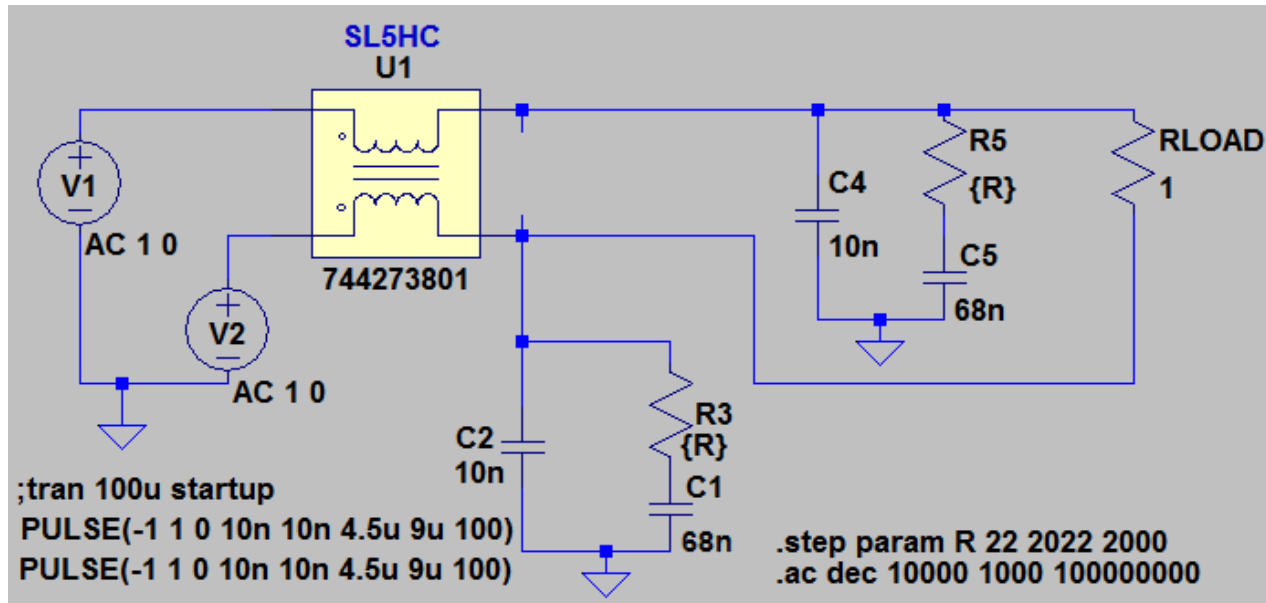


744 273 801

**CMC w Chassis**


- Power Supply Switching Frequency Considerations (L)
- EMI Higher Frequency Considerations (Z)
- Layout and Tracking
- Capacitor with and without Damping

# Common Mode Filter Design

## DM (Leakage) Effect

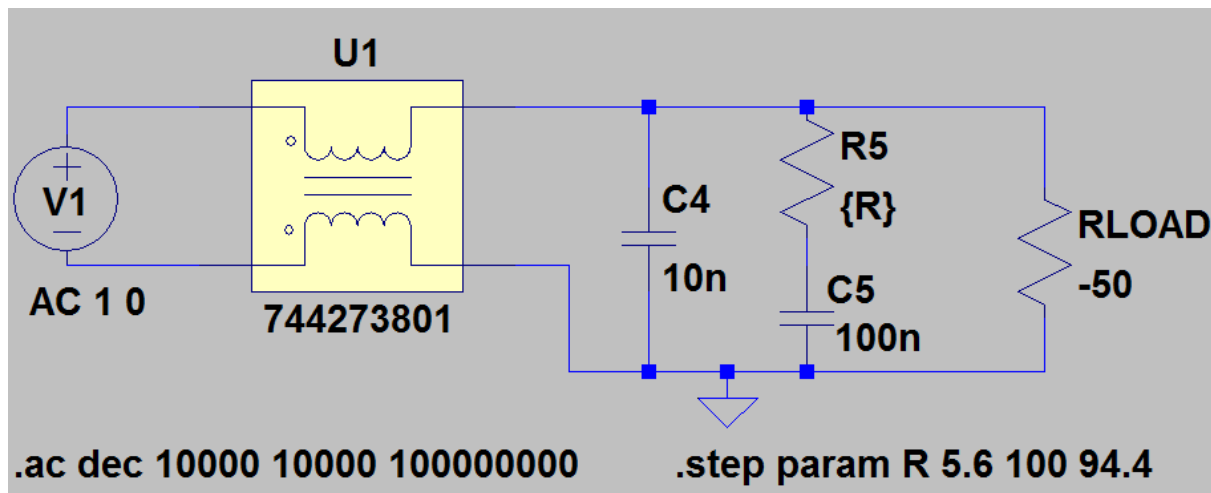

- Load Impact
- Capacitor Damping

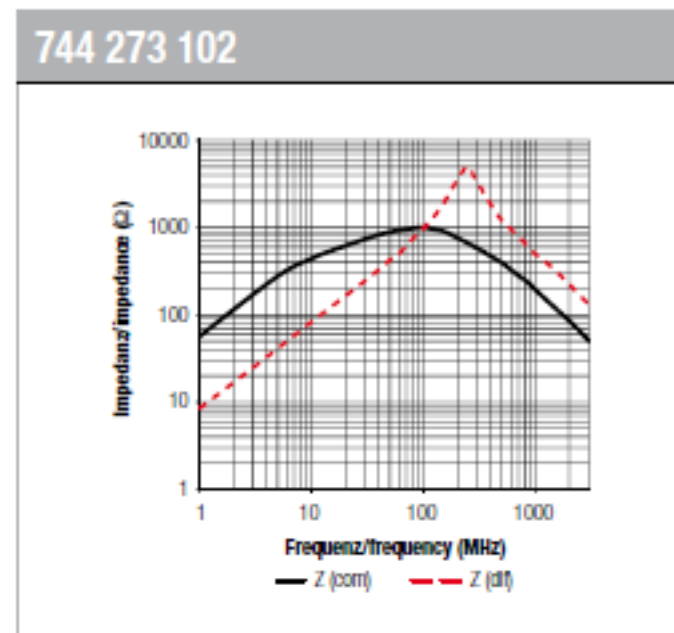


744ZF102



CMC DM Effect
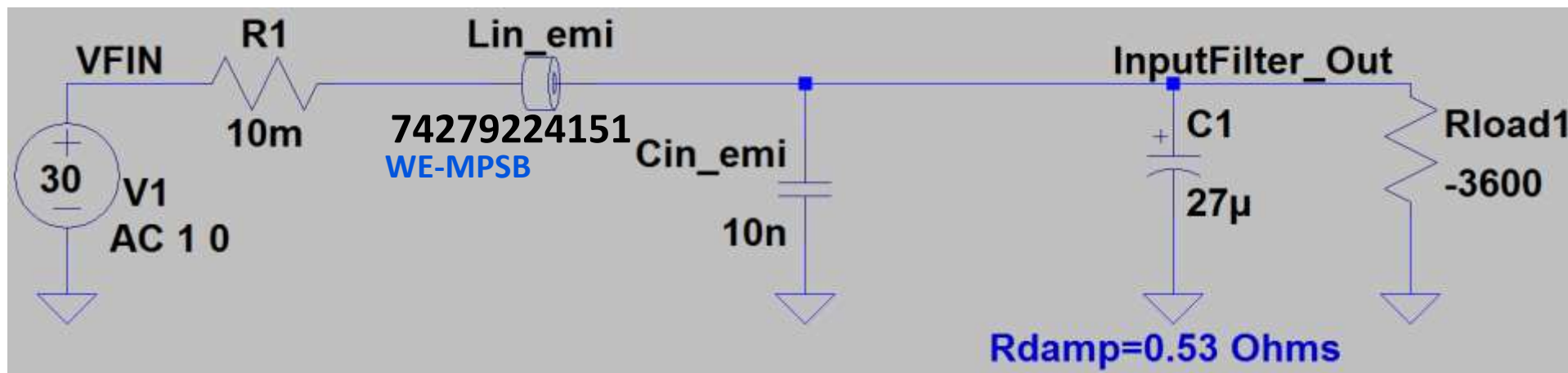
# Differential Mode Filter Design – Input




- Load Impact
- EMI Higher Frequency Considerations
- Pulse Rating (WE-MPSB)
- Layout and Tracking
- Capacitor Damping and Stability




Buck Filter AC  
Analysis



742 792 241 51

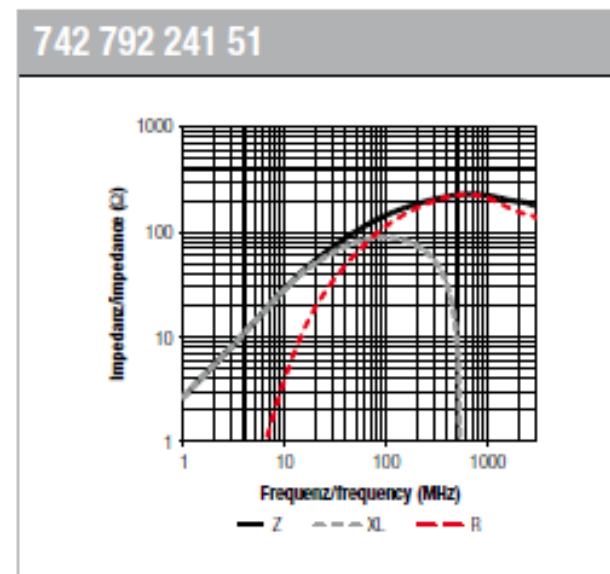

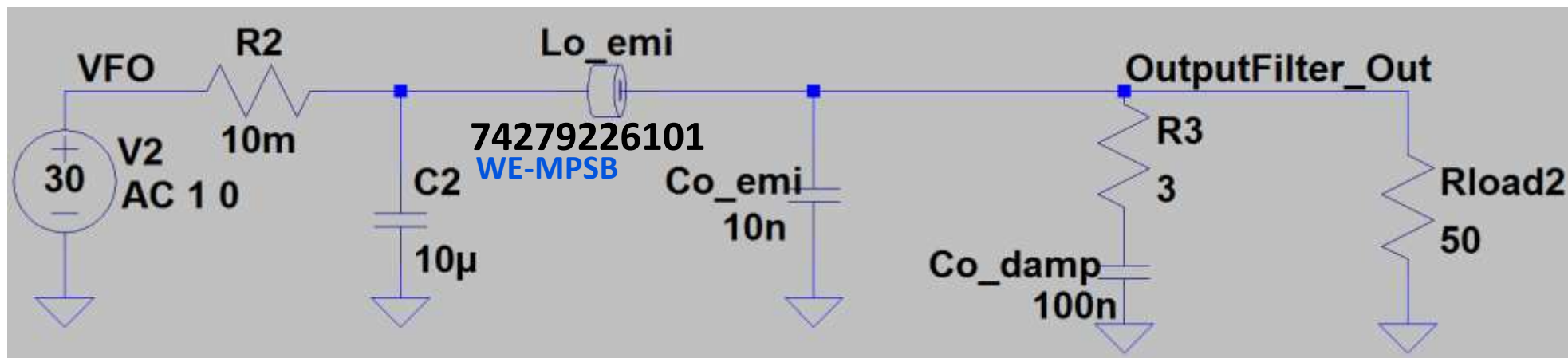
# Differential Mode Filter Design – Output




- Load Impact
- EMI Higher Frequency Considerations
- Pulse Rating (WE-MPSB)
- Layout and Tracking
- Capacitor Damping




742 792 261 01

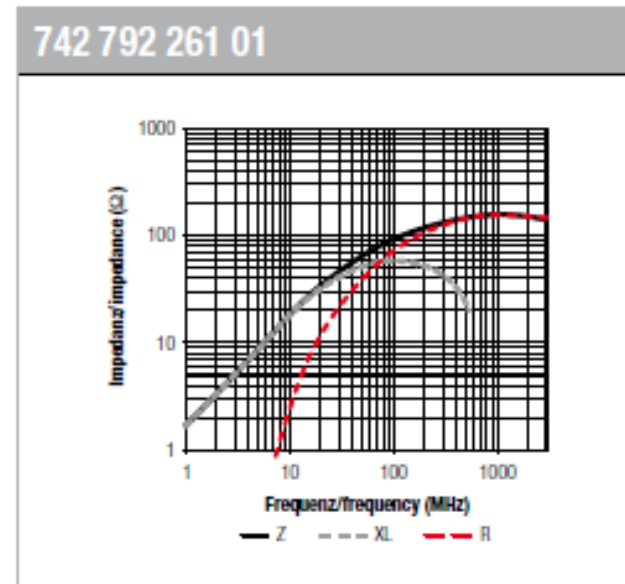
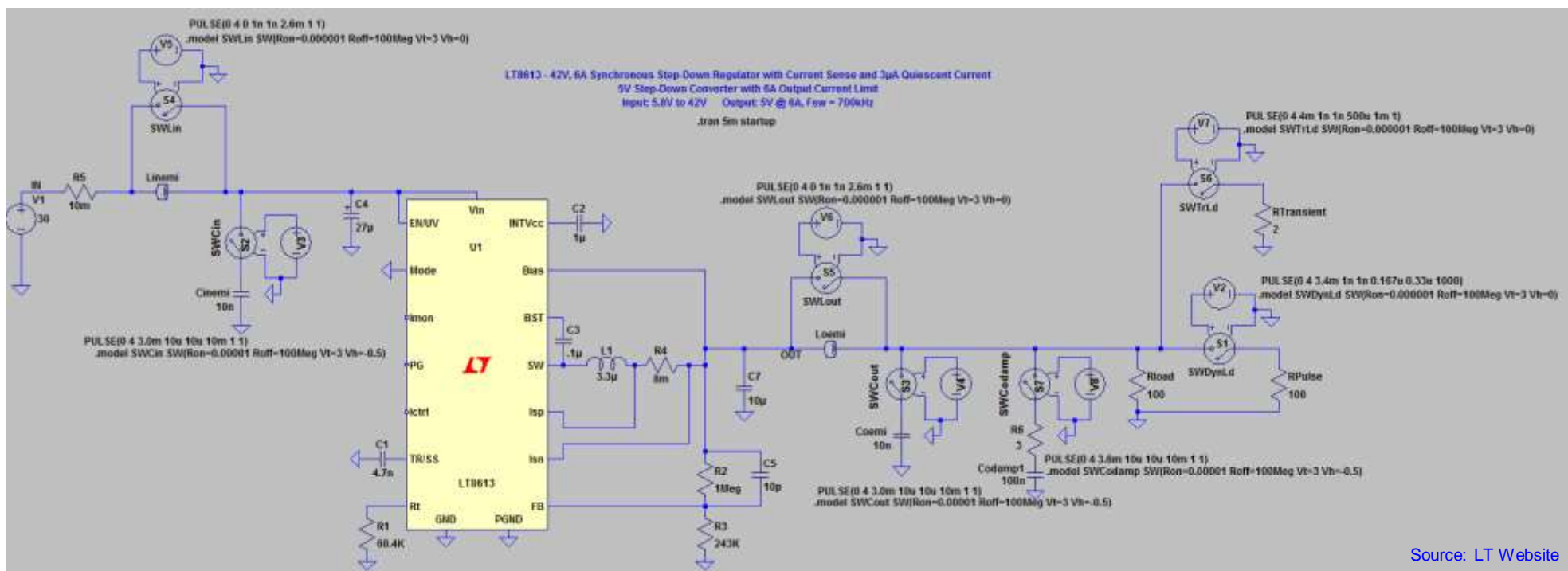
# Differential Mode Filter Design – Buck Example




## Start Up Conditions:

- No EMI Filters on I/P or O/P
- Max  $V_{in} = 30V$
- $V_{out} = 5V$ , Min Load 50mA (DCM)
- Actual filter component models used (no ideals)




# Differential Mode Filter Design – Buck Example

## Simulation Timeline

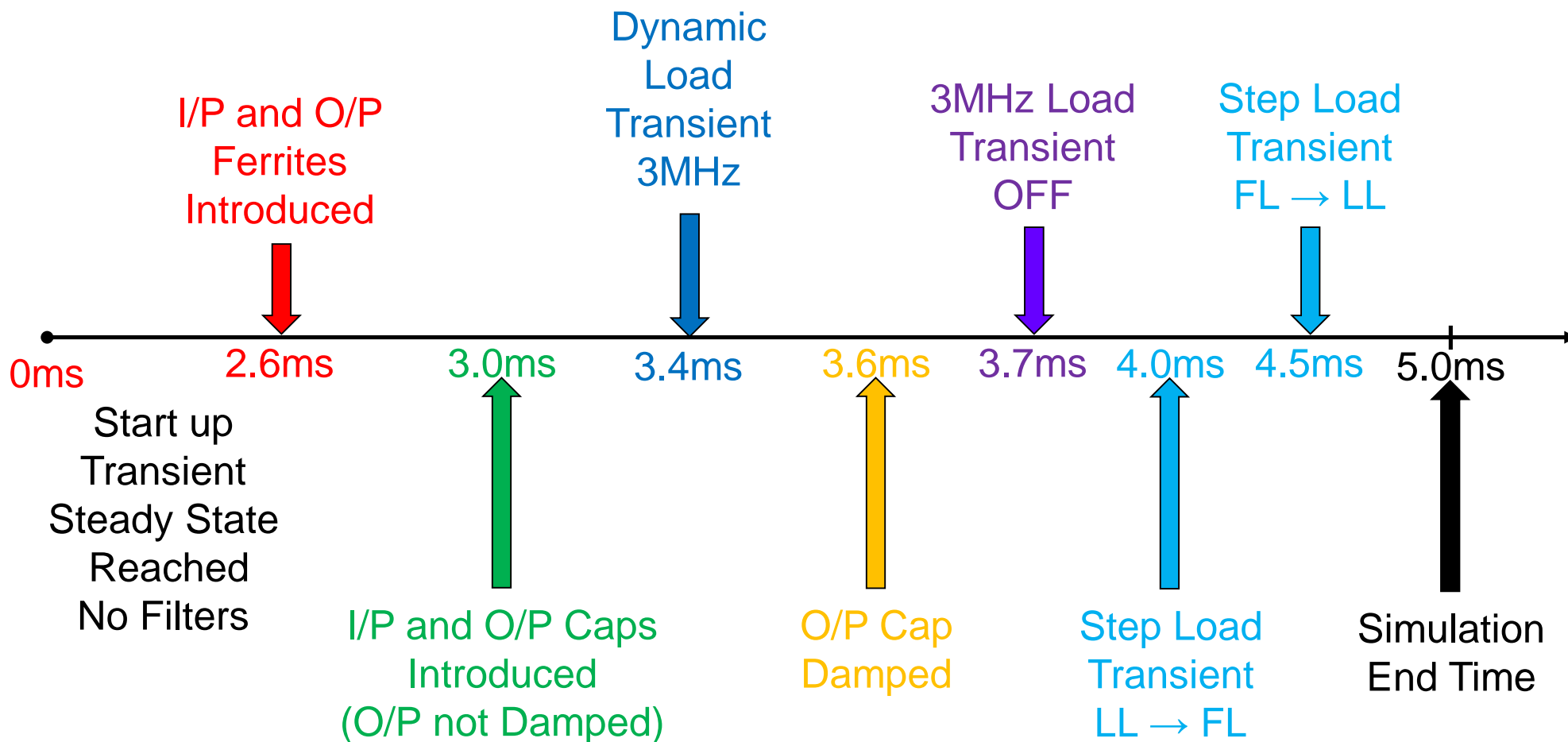

# Differential Mode Filter Design – Buck Example

## Output Voltage

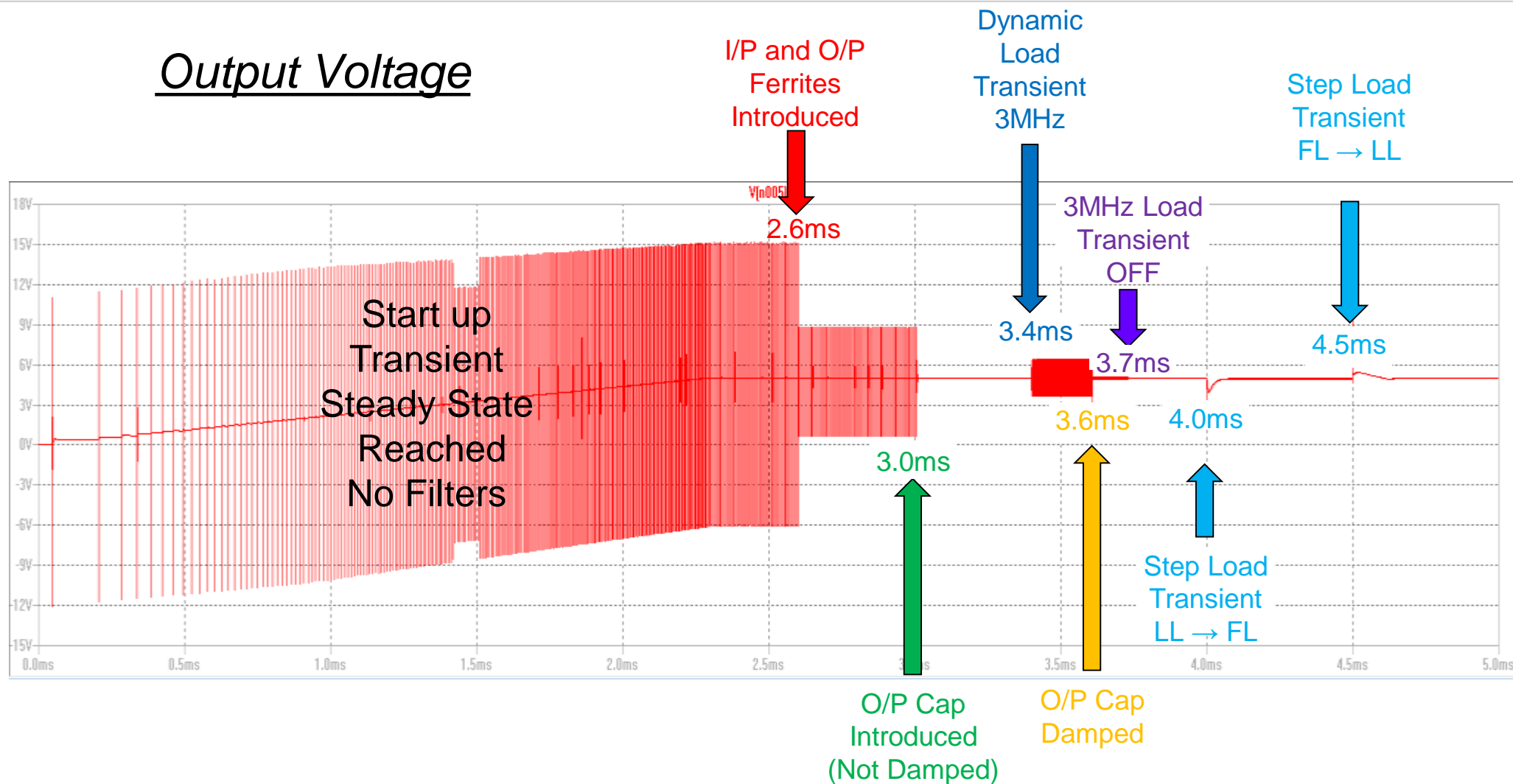







Differer


# Design – Buck Example

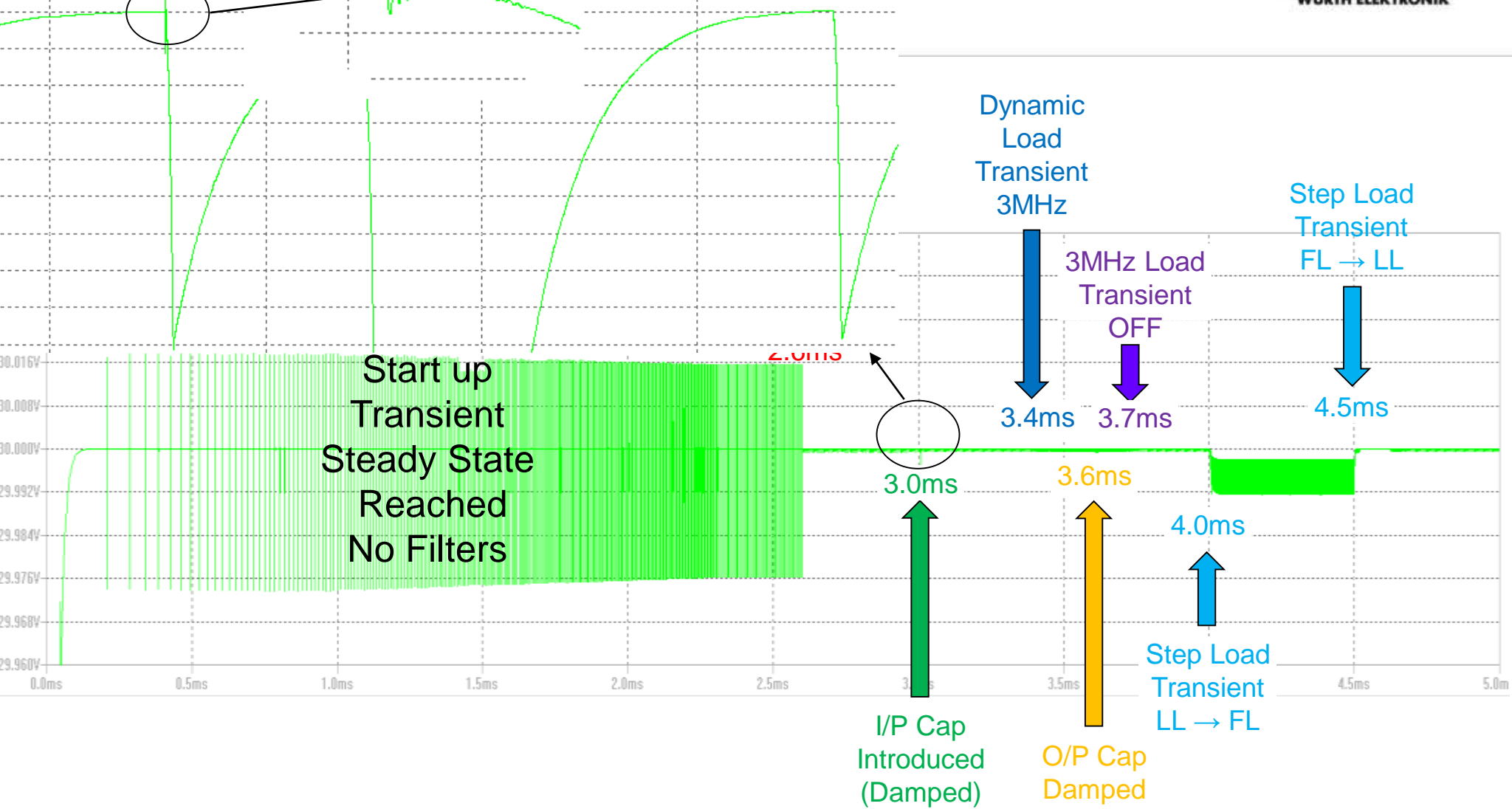
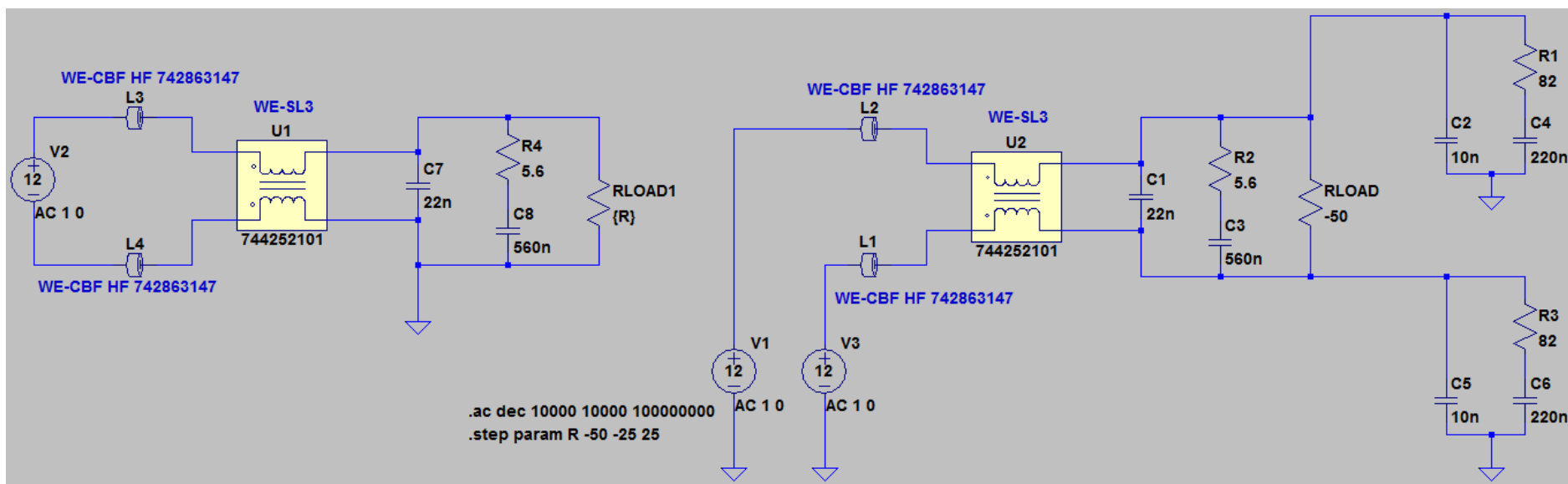
# EMI Filter Design – Recommended Architecture




742 863 147

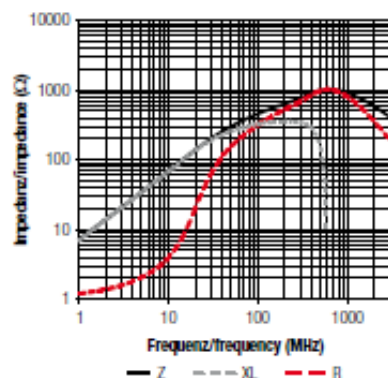


EMI/DM/CM  
Input Filter



744 252 101

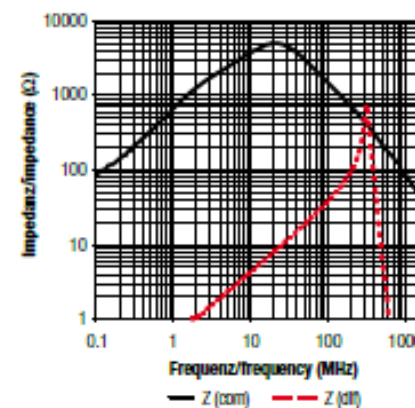

# Thank you

## Any Questions

