


By JOHN CLARKE



Unflued gas heaters are a hazard to health and life . . .

Build an Air Quality Monitor to ensure your safety and well-being

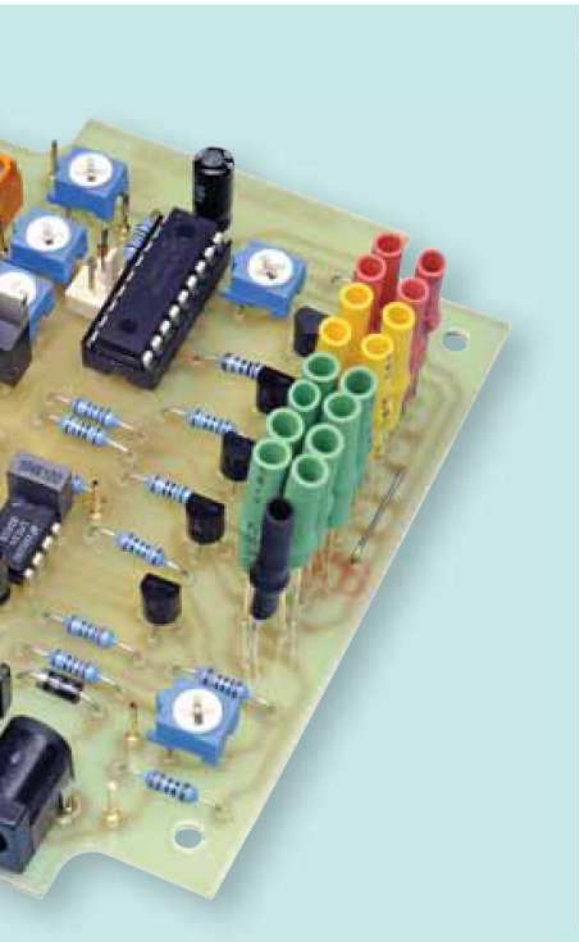This Air Quality Monitor indicates carbon dioxide (CO₂) and carbon monoxide (CO) levels on a dual bargraph, and sounds an alarm when either level reaches a preset concentration. You should use it if you have an unflued heater in your home, boat, caravan or any indoor space.



Main Features and Specifications

Features

- Detects carbon monoxide (CO) and carbon dioxide (CO₂) levels
- 15-level LED bargraph display for each gas
- Three-stage alarm ranging from initial warning through to urgent
- Internal fan replenishes air for sensors
- Automatic display dimming in low light levels

Specifications

CO₂ range: 0.03% to 1% (300-10,000ppm) with recommended calibration

CO range: 0.003% to 0.03% (30-300ppm) with recommended calibration

Bargraph displays: separate bargraphs to show CO and CO₂ concentrations, each consisting of eight LEDs with 15 display levels.

Alarm modes: 16ms chirp every 16s (third top LED), 32ms chirp every 4s (second top LED) and 64ms chirp every 0.5s (top LED).

CO₂ sensor heating: continuous at 200mA.

CO sensor heating: 60s heating at 150mA; 90s reading period at 42mA.

Readings update: CO = 2.5 minutes; CO₂ = after an initial 60s, then with a nominal 5s lag due to sensor response.

Dimming range: 205 brightness levels.

Diagnostic display: CO sensor only when VR4 is set to give 0V on TP4. The top two LEDs are lit during the heating cycle, while the third top LED and LEDs below light for the measurement cycle, with these LEDs extinguishing successively every 15s.

Power supply: 12V DC 500mA plugpack.

ALL COMBUSTION heaters, including those using wood, coal, coke, kerosene, methylated spirits and gas, draw oxygen from the air as the fuel is burnt. If used indoors, such as inside a house, this gradually reduces the oxygen concentration in the air unless there is sufficient ventilation to the outside. However, judging how much room ventilation is needed to keep the air safe is almost impossible, and it's all too easy to provide insufficient outside air. After all, you do want to keep warm.

If you don't have sufficient fresh air in the room, there is the immediate danger that the deadly gas carbon monoxide will be produced. This is much more likely if the heater is unflued, whereby the combustion gases are released into the room. Many gas heaters are unflued, and every one of these is a potential source of carbon monoxide and other noxious gases.

Not the answer

Some gas heater designs attempt to get around this problem by employing an

oxygen depletion sensor. These extinguish the heater if the oxygen concentration in the room is reduced by 20%. While better than having no sensor at all, this definitely should not be regarded as a safe answer.

Why? Because regardless of whether the oxygen depletion sensor, a pretty crude device, is working, the heater may still produce some carbon monoxide as well as the normal combustion products of carbon dioxide, water vapour, nitrogen oxides, sulphur dioxide and formaldehydes.

An oxygen depletion sensor does not detect or react to any of these noxious and potentially harmful gases – it only detects a reduction in oxygen concentration.


Even if no carbon monoxide is produced, all unflued gas heaters still produce the other combustion products listed above, and these can cause breathing difficulties for people who suffer from asthma or allergies. Ultimately, unflued gas heaters must be regarded as less than ideal, but they are much cheaper than properly flued

gas heaters and most of them have the advantage of using a bayonet gas connector, which allows them to be moved from room to room.

Monitoring air quality

Ideally, if you have a combustion heater in your home, there should be some means of monitoring the air quality. This is where the Air Quality Monitor comes in, it measures both carbon dioxide and carbon monoxide levels, and displays the results on LED bargraphs. If the concentration of either of these gases rises above a preset level, a loud alarm will sound, which means that you should turn off the heater and open the room up to fresh air.

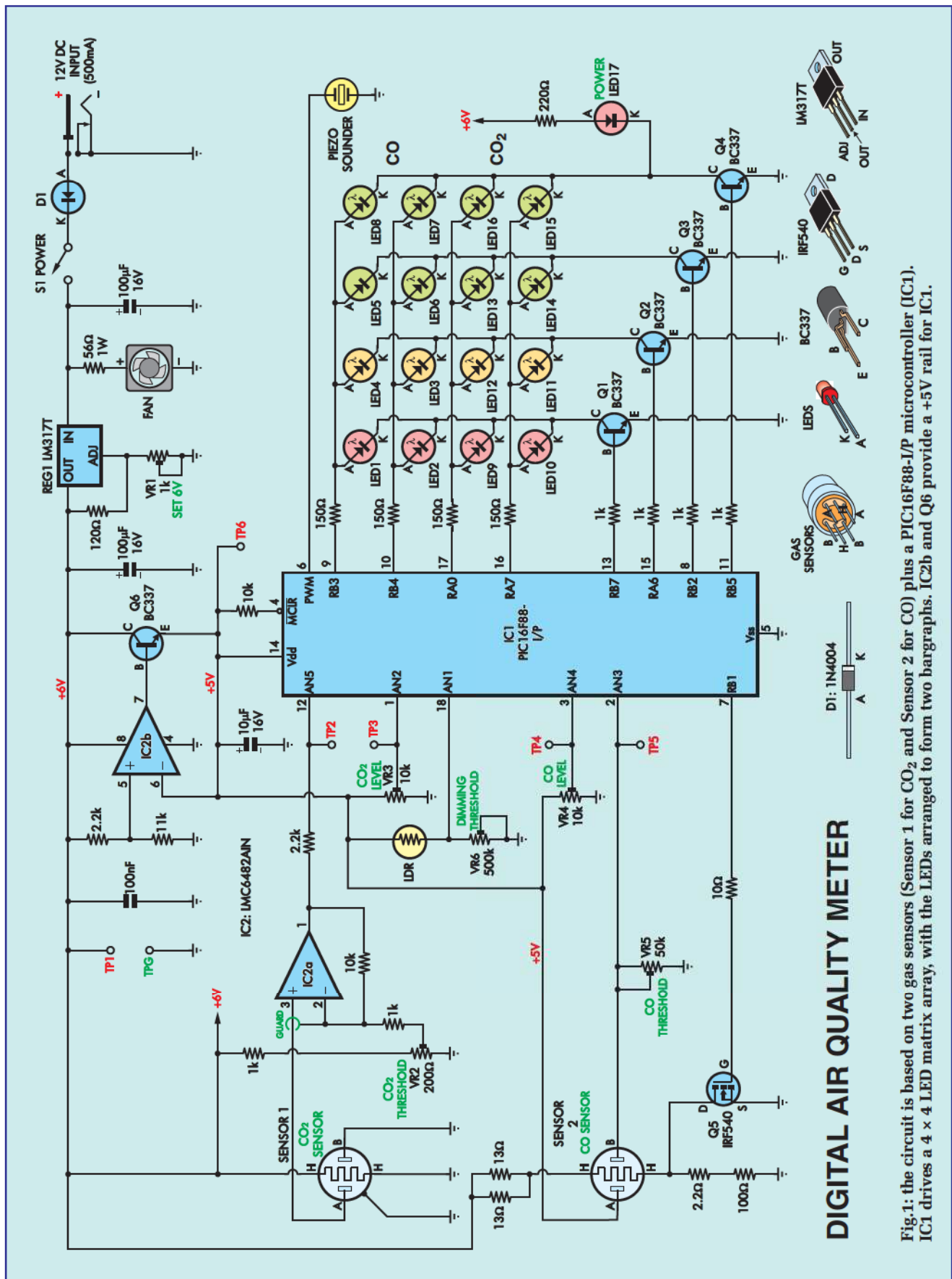Each bargraph comprises eight LEDs that light individually (ie, one at a time) to show eight distinct levels. In-between values are displayed by lighting two adjacent LEDs. This gives a total of 15 levels that can be displayed. The four lower LEDs are green, followed by two orange and then two red LEDs. An automatic



dimming circuit ensures that the LED displays are not too bright at night.

In addition, the alarm sounds if any of the top three LEDs light in either display. There are three alarm levels:

- 1) Main alarm sounds if the top LED lights. This consists of a 64ms-long 4kHz tone that repeats every 0.5s
- 2) Less urgent alarm sounds if the second top LED is lit (top LED off). This alarm gives a 32ms-long 4kHz 'chip' every four seconds (4s)
- 3) Warning alarm sounds if the third top LED is alight. This alarm mode gives a brief 16ms 4kHz 'chirp' every 16 seconds (16s).

As shown in the photos, the Air Quality Monitor is housed in a plastic case with a clear lid to reveal the LED bargraphs. An internal fan at one end draws air through the box so that the internally mounted CO and CO₂ sensors are presented with a continuous sample of the air that's being monitored. Power for the unit comes from a 12V DC 500mA plugpack.

Circuit details

Take a look now at the Air Quality Monitor circuit of Fig.1. It's based on two gas sensors and a PIC microcontroller (IC1). The microcontroller monitors the sensor signals and drives two multiplexed LED bargraph displays.

We'll start by looking at the CO₂ sensor. This consists of a heater coil and a solid electrolyte cell comprising a lithium (Li) cathode and a potassium (Ka) anode. When these electrodes react with carbon dioxide, a potential difference is produced between them that varies with the CO₂ concentration.

The sensor is built into a metal housing and is exposed to air (and to CO₂) via a stainless steel mesh. Its output in normal air (ie, with a normal CO₂ concentration) is typically 325mV. This voltage falls with increased CO₂ concentrations beyond 400ppm (parts per million) or 0.04%.

The CO₂ concentration in normal air is 0.0314%, but this can increase to 5% in air that's directly exhaled from the lungs. At this latter level, the sensor's output will be well below 250mV (compared to 325mV in standard air).

The CO₂ sensor's output appears across its 'A' and 'B' terminals, and has a very high impedance, so any loading will drastically reduce this output. As a result, the manufacturer

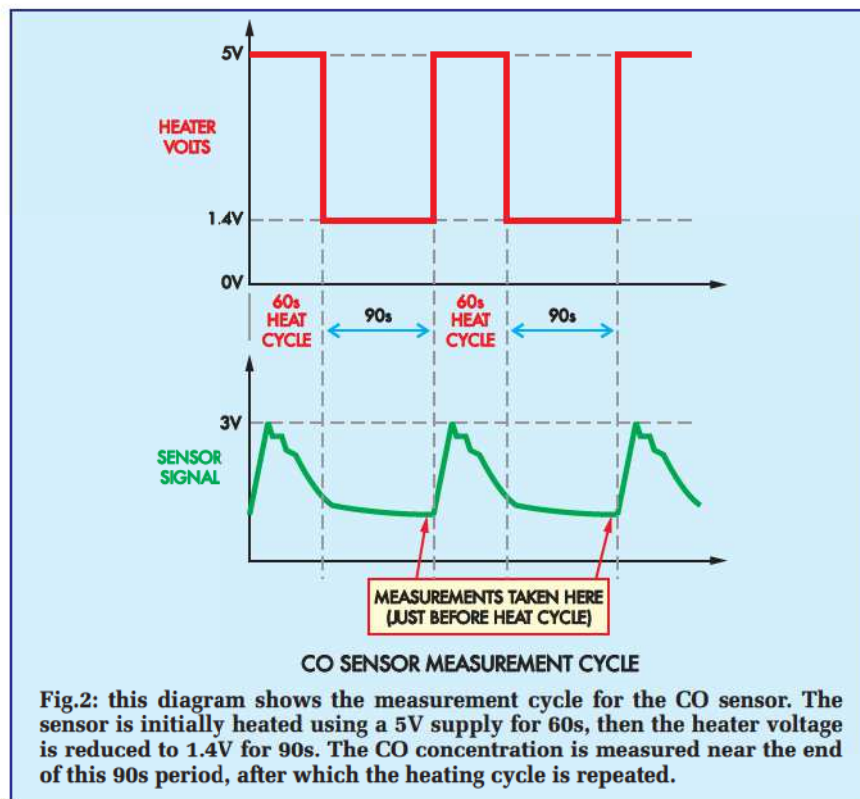


Fig.2: this diagram shows the measurement cycle for the CO sensor. The sensor is initially heated using a 5V supply for 60s, then the heater voltage is reduced to 1.4V for 90s. The CO concentration is measured near the end of this 90s period, after which the heating cycle is repeated.

recommends monitoring the voltage using a circuit that has a 100GΩ to 10TΩ input impedance and an input current not exceeding 1pA.

To comply with these requirements, we have used an LMC6482 CMOS op amp (IC2a) to buffer the sensor signal. Its input impedance is 10TΩ, while the input current is typically just 0.02pA.

Note, however, that these specifications would not normally be met when the op amp and the sensor are mounted on a PC board, due to leakage current. Fortunately, this leakage current can be prevented by shielding the sensor's output pin and the op amp's pin 3 input with a complete loop of copper track.

As shown, this loop is connected to the op amp's pin 2 inverting input. Because the inverting input is at the same potential as the non-inverting input, no current flows between them and the shield (or guard) track prevents any leakage between pin 3 and other sections of the PC board.

CO₂ threshold

IC2a is wired as a non-inverting stage with a gain of about 11, as set by the 10kΩ and 1kΩ feedback resistors. As a result, a 315mV output from the sensor (ie, in normal air) should

result in a 3.47V output from the op amp.

In practice, we found that the output from the particular CO₂ sensor we used was greater than 315mV in normal air, causing IC2a's output to go above 5V. Consequently, trimpot VR2 has been added so that IC2a's output can be level shifted, to correctly set the output to 3.47V in normal air.

Note that VR2 changes IC2a's gain slightly, depending on its setting, but this doesn't matter in this application.


In practice, VR2 is adjusted so that the lowest LED in the CO₂ bargraph is just off in normal air. By contrast, the maximum bargraph level is adjusted using trimpot VR3, which sets the voltage on the AN2 (pin 1) input of IC1. This voltage is used by IC1 to calculate the display levels.

The amplified sensor signal at the output of IC2a is applied to the AN5 (pin 12) input of IC1 via a 2.2kΩ resistor. An internal analogue-to-digital (A/D) converter then converts the signal to a digital output to drive the bargraph display.

Note that the output from the sensor is valid only after it has been heated sufficiently. This is achieved by connecting a 6V supply across the internal heater element.

Constructional Project

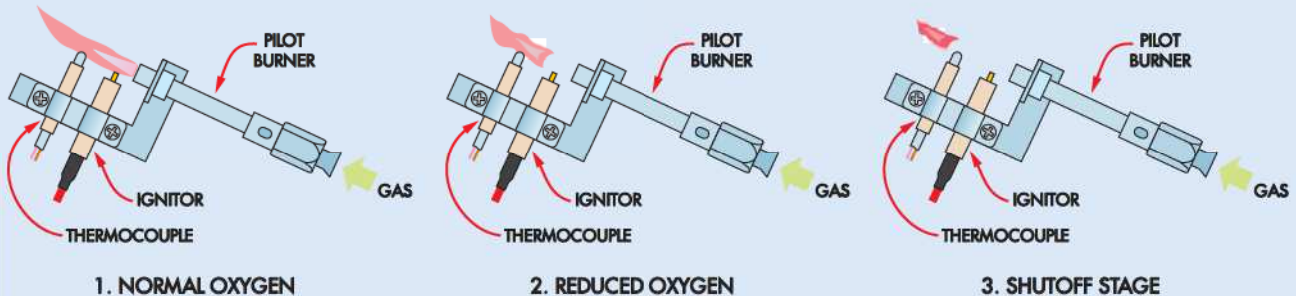How an oxygen depletion sensor (ODS) works



1. **NORMAL OXYGEN**

An oxygen depletion sensor consists of a pilot burner, a thermocouple and an ignitor. When the oxygen level in the air is normal (20.9%), the pilot flame touches the tip of the thermocouple as shown at (1). As a result, the thermocouple generates a

voltage which indirectly activates an electromagnet and keeps the heater's gas valve open.

When the oxygen level decreases to around 19%, the pilot flame begins to lift and the thermocouple begins to cool (2). Finally, at 18% oxygen, the unstable

pilot flame lifts off the thermocouple and its output voltage decreases (3). At that point, the electromagnet closes the gas valve and the heater ceases operation.

The heater can only be restarted when the oxygen level in the room returns to normal.

The effects of CO and CO₂

Carbon monoxide (CO) is a colourless, odourless gas that's made up of molecules comprising one carbon (C) atom and one oxygen (O) atom. By contrast, carbon dioxide (CO₂) molecules consist of one carbon and two oxygen atoms. Over time, CO molecules will pair with a spare oxygen atom to form the more stable carbon dioxide (CO₂) gas.

CO₂ has a concentration of about 0.03% in fresh air and is not dangerous at such low levels. However, higher concentrations result in accelerated breathing, and an increase in heart rate, and can lead to headaches and dizziness. And a concentration of 10% can cause respiratory failure and death within a matter of minutes.

CO₂ concentrations can increase in enclosed spaces when oxygen is combined with carbon to form CO₂, due to combustion and respiration. High CO₂ concentrations are a sure sign that oxygen has been depleted from the air and this can heighten the adverse effects of elevated CO₂ levels.

Poor combustion can result in the production of the oxygen-starved carbon monoxide (CO) gas. Carbon monoxide is extremely dangerous because it has a 200-times greater affinity for haemoglobin than oxygen. As a result, it blocks oxygen from being carried by the blood supply to other parts of the body, including the brain.

Table 3 lists the physiological effects of various concentrations of carbon monoxide in air. As can be seen, even relatively low concentrations can be dangerous.

Table 3: Physiological effects of CO

Concentration	Symptoms
0.005% (50ppm)	No symptoms with prolonged exposure
0.01% (100ppm)	Slight headache within a few hours
0.05% (500ppm)	Headache within 1 hour, increasing in severity over time
0.1% (1000ppm)	Headache, dizziness and nausea within 20-30 minutes; death within two hours
0.4% (4000ppm)	Headache, dizziness and nausea within 5-10 minutes; death within 30 minutes
1% (10,000ppm)	Death in 1-3 minutes

For this reason, the microcontroller ignores readings from this sensor for the first 60s after power is applied.

CO sensor

The output from the CO sensor (Sensor 2) is monitored at the AN3 input (pin 2) of IC1. However, this sensor operates differently from the CO₂ sensor, in that it varies its resistance with CO concentration.

The sensor is made up of a tin dioxide layer deposited onto an aluminium oxide ceramic tube. This tube is fitted inside a plastic housing and is exposed to air (and CO) via a stainless steel mesh.

The specifications state that this sensor must initially be heated using a 5V supply connected across its heater element for 60s. The heater current is then reduced by placing just 1.4V across the element for a 90s period. The CO concentration is then measured, after which the initial 60s heating cycle begins again – see Fig. 2.

In practice, this means that measurements are repeated at 2½ minute (150s) intervals.

In our circuit, the heater is powered from a +6V rail via two parallel 13Ω resistors (equivalent to 6.5Ω), while MOSFET Q5 ties the lower end of the heater element to 0V. The heater has a resistance of 33Ω, so when Q1 is on, a current of 152mA flows through it. This results in a 1V drop across the two 13Ω resistors, thus giving the required 5V supply for the heater.

Q5 is controlled by IC1's RB1 output (pin 7) and turns on when its gate is pulled high. In operation, RB1 switches Q5 on for 60s to provide the heating current. RB1 then goes low for 90s, which switches Q5 off, so that the measurement can be made.

During this 90s period (ie, with Q5 off), the CO sensor's heater is effectively in series with the 2.2Ω and 100Ω resistors connected across Q5. As a result, the current through the sensor drops to 42.34mA, which means that the voltage across the heater is now 1.397V (ie, 33 × 0.4234). That is close enough for practical purposes to the 1.4V value specified.

As before, the sensor's output appears across its A and B terminals. This output varies in resistance according to CO concentration, so one side is connected to the +5V rail and the other side to 0V via trimpot VR5 to form a voltage divider.

As a result, any changes in the sensor's resistance (ie, due to CO variations) will result in a corresponding voltage change at the top of VR5. This signal is then applied to the AN3 input of IC1 (pin 2) and fed to its internal A/D converter.

During set-up, VR5 is set so that AN3 is at 0.5V when the sensor is in normal air. However, this signal voltage can rise to around 3V when the CO concentration is over 300ppm.

In operation, the sensor varies its resistance over a 10:1 range for CO concentrations ranging from 10ppm to 1000ppm.

The maximum bargraph level for CO is adjusted using trimpot VR4. It effectively forms a voltage divider across the 5V supply, and its output is applied to the AN4 (pin 3) input of IC1. This voltage, along with the sensor voltage on AN3, is then used by IC1 to calculate the bargraph display level.

Bargraphs

Two 8-LED bargraphs are used to indicate the CO₂ and CO levels, and these are driven via eight outputs from IC1. These 16 LEDs (LED1 to LED16) are wired in a 4 × 4 matrix, with transistors Q1 to Q4 driving their common cathode (K) connections. Q1 to Q4 are in turn driven by the RB7, RA6, RB2 and RB5 outputs of IC1 via 1kΩ resistors.

In greater detail, transistor Q1 drives the cathodes (K) of LED1, LED2, LED9 and LED10, while their anodes (A)

Parts List – Air Quality Monitor

1 PC board, code 834, available from the <i>EPE PCB Service</i> , size 104mm × 78mm	1 340mm length of black 5mm heatshrink tubing; OR
1 ABS box with clear lid, 115mm × 90mm × 55mm (Jaycar HB-6246 or equivalent)	1 160mm length of 5mm green heatshrink tubing, 1 80mm length of 5mm yellow heatshrink tubing and 1 100mm length of 5mm red heatshrink tubing (to match LED colours)
1 front panel label, 84mm × 80mm, printed onto clear plastic film (eg, overhead projector film)	
1 CO sensor (Jaycar RS-5615 or equivalent)	Semiconductors
1 CO ₂ sensor (Jaycar RS-5600 or equivalent)	1 PIC16F88-I/P programmed microcontroller (IC1)
1 50kΩ LDR with >1MΩ dark resistance (Jaycar RD-3480 or equivalent)	1 LMC6482AIN dual op amp (IC2)
1 12V DC 500mA plugpack	5 BC337 transistors (Q1-Q4, Q6)
1 12V cooling fan, 40mm × 40mm × 10mm	1 IRF540-N channel MOSFET (Q5)
1 piezo transducer, 30mm diameter	1 LM317T adjustable voltage regulator (REG1)
1 2.5mm PC-mount DC power socket (CON1)	1 1N4004 1A diode (D1)
1 SPDT PC-mount miniature toggle switch (S1)	5 3mm red LEDs (LEDs 1 to 2, LEDs 9 to 10, LED17)
1 2-way screw terminal block, 5.08mm pin spacing (CON2)	4 3mm orange LEDs (LEDs 3 to 4, LEDs 11 to 12)
1 2-way male pin header, 2.54mm pin spacing	8 3mm green LEDs (LEDs 5 to 8, LEDs 13 to 16)
1 2-way female pin header, 2.54mm pin spacing	Capacitors
1 18-pin IC socket	2 100μF 16V radial elect.
1 mini TO-220 finned heatsink, 19mm × 19mm × 9.5mm	1 10μF 16V radial elect.
2 M4 × 12mm countersunk (CSK) screws (to secure fan)	1 100nF MKT (code 100n or 104)
2 M3 × 10mm countersunk screws (to secure piezo transducer)	Resistors (0.25W 1%)
1 6mm ID (internal diameter) nylon washer (spacer for piezo transducer)	1 11kΩ 1 120Ω
4 M3 × 6mm screws	2 10kΩ 1 100Ω
1 M3 × 10mm screw	2 2.2kΩ 1 56Ω 5% 1W
1 M3 nut	6 1kΩ 2 13Ω
1 60mm length of 0.7mm tinned copper wire	1 220Ω 1 10Ω
8 PC stakes	4 150Ω 1 2.2Ω 5%
	Trimpots
	1 500kΩ miniature horizontal trimpot (VR6)
	1 50kΩ miniature horizontal trimpot (VR5)
	2 10kΩ miniature horizontal trimpot (VR3,VR4)
	1 1kΩ miniature horizontal trimpot (VR1)
	1 200Ω miniature horizontal trimpot (VR2)

are respectively driven via the RB3, RB4, RA0 and RA7 outputs via 150Ω limiting resistors. Similarly, transistor Q2 drives the cathodes of the second LED column in the matrix, Q3 the third column cathodes and Q4 the fourth column cathodes.

In operation, the LED bargraphs are controlled in multiplexed fashion, with

the transistors switched on one at a time in turn. This allows the LEDs in a switched column to be lit individually.

For example, when Q1 is switched on, either LED1, LED2, LED9 or LED10 can be switched on. This is done by taking either RB3, RB4, RA0 or RA7 of IC1 high. Alternatively, by taking more than one of these outputs high,

Constructional Project

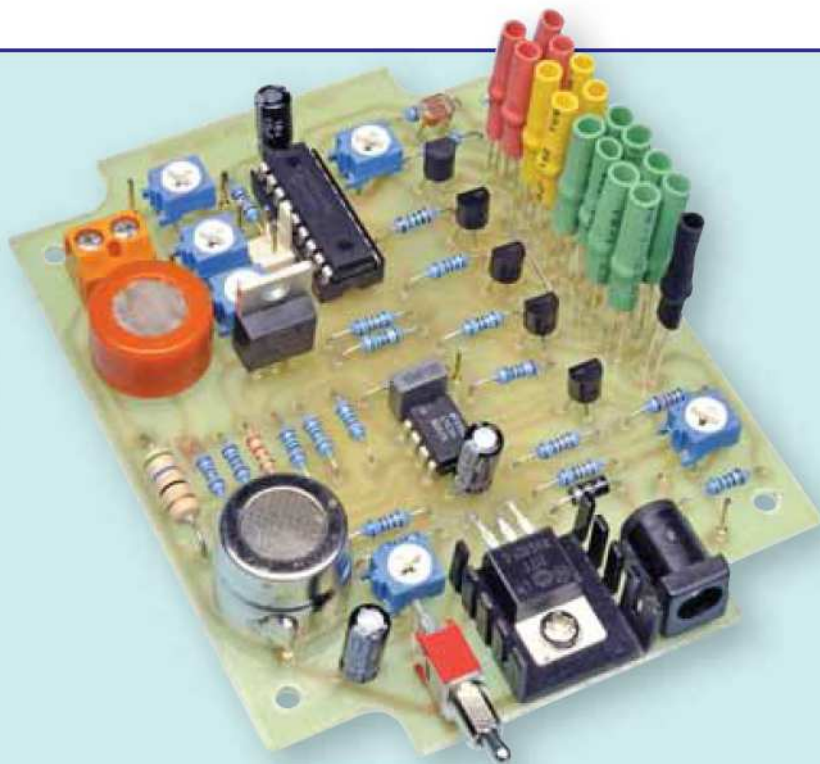
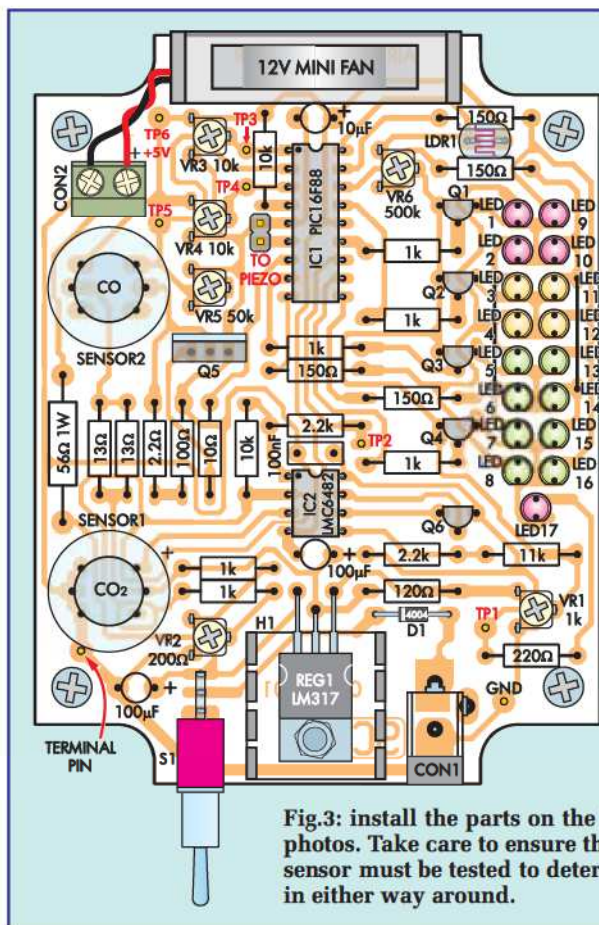


Fig.3: install the parts on the PC board as shown in this layout diagram and the accompanying photos. Take care to ensure that all polarised parts are correctly oriented, and note that the CO₂ sensor must be tested to determine its polarity before it is fitted (see text). The CO sensor can go in either way around.

the LEDs can be switched on in any combination.

The same goes for the other columns in the matrix when their switching transistor is on.

Each transistor is driven on for about 1ms before switching off. As soon as it switches off, the next transistor is switched on to drive the next column of LEDs. However, there is a short gap (or 'dead time') between one transistor switching off and the other switching on, to prevent display errors.

In operation, the LEDs are switched on and off at such a fast rate that they appear to be continuously lit. They are also physically laid out on the PC board as two bargraph columns. The top two rows of LEDs in the matrix (LED1 to LED8) form the CO bargraph, while the bottom two rows (LED9 to LED16) form the CO₂ bargraph.

LED17 is the power on indicator. This connects to the +6V supply via a 220Ω current-limiting resistor, and is driven by transistor Q4 so that it always appears lit when power is applied.

Display dimming

Automatic display dimming is achieved using a light-dependent resistor (LDR). As shown, the LDR is connected in series with trimpot VR6 across the 5V supply to form a voltage divider. The output of this voltage divider is connected to the AN1 input (pin 18) of IC1.

In bright light, the LDR's resistance is 50kΩ or less, and so the voltage applied to IC1's AN1 input is pulled close to the 5V supply. This signals IC1 to drive the LEDs at full brightness.

Conversely, at lower ambient light levels, the LDR's resistance increases and the voltage at AN1 decreases. As a result, IC1 now drives the LEDs with a reduced duty cycle. This is achieved by using a longer dead time, ie, the time between when one transistor switches off and the next one switches on. This effectively reduces the length of time that the LEDs are lit and hence reduces their brightness.

In full darkness, the LDR has a high resistance and VR6 pulls the AN1 voltage down close to 0V. The display is then dimmed to its maximum extent.

Piezo alarm

The alarm feature is provided by using the pin 6 PWM (pulse-width modulation) output of IC1 to drive a piezo transducer. Its frequency of operation is set to 4kHz (50% duty cycle) and there are three alarm modes, as described earlier.

Note that the alarm is only activated when one of the top three LEDs in either bargraph is lit.

Power supply

Power for the circuit is derived from a 12V DC 500mA plugpack, with diode D1 providing reverse polarity protection. The nominal +12V supply rail is then fed via on/off switch S1 to the input of a 3-terminal voltage regulator, REG1, with filtering provided by a 100µF 16V electrolytic capacitor.

This +12V supply rail also drives a 12V fan via a 56Ω resistor. The resistor is there to reduce the fan speed and thus the noise it makes, while still allowing sufficient air to be drawn through the monitor case.

REG1 is an LM317T variable regulator, and is configured to provide a 6V

Constructional Project



Above: inside the completed prototype. Light pipes made from heatshrink sleeving are fitted to the bargraph and power LEDs.

supply. The voltage between its OUT and ADJUST pins is nominally 1.25V, but in practice can be anywhere from 1.2V to 1.3V.

If this voltage is 1.25V, this means that a current of 10.4mA flows through the 120Ω resistor and trimpot VR1. Adjusting VR1 to 456Ω sets the voltage across it to 4.75V and the output of the regulator to 6V (ie, 4.75V

+ 1.25V). This 6V supply is used to drive the heaters in the CO₂ and CO sensors.

In addition, the 6V rail is fed to a voltage divider made up of 2.2kΩ and 11kΩ resistors. The resulting +5V output from the divider is then fed to the pin 5 (non-inverting) input of op amp IC2b, which in turn drives current amplifier Q6 (BC337).

As shown, Q6's emitter (E) provides feedback to IC2b's inverting input (pin 6). As a result, IC2b automatically adjusts its output to maintain +5V at Q6's emitter. This +5V rail powers microcontroller IC1, trimpots VR3 and VR4 and LDR1.

Software

All software program files for the *Air Quality Monitor* will be available from the EPE website at: www.epemag.com.

Construction

Construction is a snap, with all parts, except the 12V fan and piezo alarm, mounted on a single PC board. This board is coded 834 (104mm × 78mm) and is housed in a 115mm × 90mm × 55mm IP65 ABS box. It has a clear lid so that the LED bargraphs are visible. The printed circuit board is available from the EPE PCB Service.

The PC board is designed to mount onto integral standoffs within the box. Begin construction by checking that the PC board fits neatly inside this case. If not, carefully file the edges and/or file the corner cutouts until it does.

Next, check the PC board for breaks in the copper tracks or shorts between tracks and pads. Repair any defects as necessary (they are rare these days), then check that the hole sizes are correct by test-fitting the larger parts (ie, the screw terminal block, regulator REG1, trimpots, sensors and the DC socket).


Check also that the regulator's mounting hole and the corner mounting holes are all 3mm in diameter.

Fig.3 shows the parts layout on the PC board. Start the board assembly by fitting the two wire links and the resistors. The resistor colour codes are

Table 1: Resistor Colour Codes

	No.	Value	4-Band Code (1%)	5-Band Code (1%)
□	1	11kΩ	brown brown orange brown	brown brown black red brown
□	2	10kΩ	brown black orange brown	brown black black red brown
□	2	2.2kΩ	red red red brown	red red black brown brown
□	6	1kΩ	brown black red brown	brown black black brown brown
□	1	220Ω	red red brown brown	red red black black brown
□	4	150Ω	brown green brown brown	brown green black black brown
□	1	120Ω	brown red brown brown	brown red black black brown
□	1	100Ω	brown black brown brown	brown black black black brown
□	1	56Ω 1W 5%	green blue black gold	not applicable
□	2	13Ω	brown orange black brown	brown orange black gold brown
□	1	10Ω	brown black black brown	brown black black gold brown
□	1	2.2Ω 5%	red red gold gold	not applicable

Constructional Project

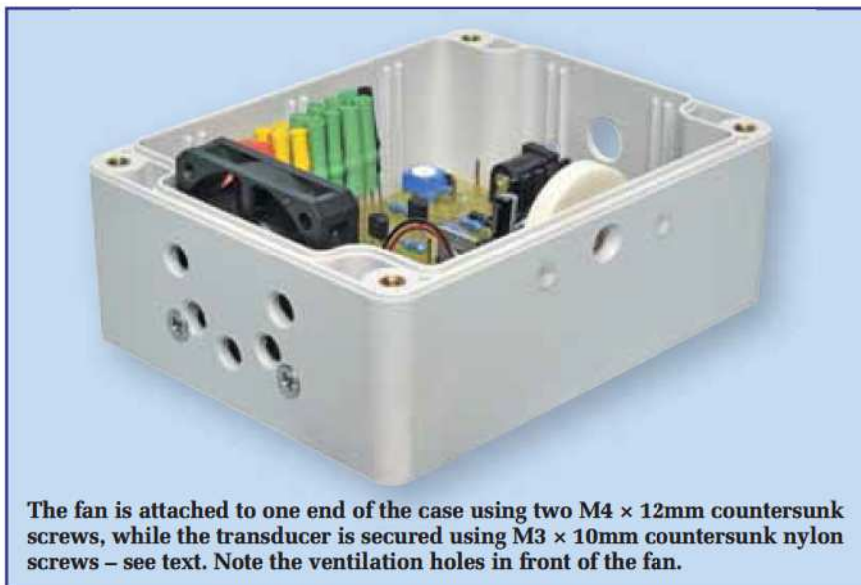

The fan is attached to one end of the case using two M4 × 12mm countersunk screws, while the transducer is secured using M3 × 10mm countersunk nylon screws – see text. Note the ventilation holes in front of the fan.

shown in Table 1, but you should also check each one with a DMM (digital multimeter) just to make sure.

Diode D1 is next on the list, take care to install it with the orientation shown. Once it's in, install PC stakes at all the test points and adjacent to the CO₂ sensor, then install the 2-way pin header for the piezo transducer.

Next, install an 18-pin IC socket for microcontroller IC1, again taking care to orient it correctly (ie, notch towards the top). By contrast, IC2 can be directly mounted on the PC board, and this can go in next. It faces in the same direction as IC1.

The DC socket and the 2-way screw terminal block are next on the list. Be sure to mount the latter with its access holes facing outwards. Transistors Q1 to Q4 and Q6 (all BC337) can then be installed.

Follow these parts with MOSFET Q5 (IRF540). This is mounted vertically with its metal tab towards trimpot VR5 and doesn't require a heatsink.

CO₂ sensor orientation

The CO₂ sensor has a symmetrical pin arrangement and hence will fit the PC board either way around. However, there's nothing on the package to indicate which output is the positive terminal.

This means that the sensor's output has to be checked before it is soldered in place on the PC board. Be sure to follow the step-by-step procedure in the text before fitting this device.

By contrast, regulator REG1 mounts horizontally on the PC board and must be fitted with a small U-shaped TO-220 finned heatsink for cooling.

To install REG1, first bend its two outer leads down through 90° about 7mm from its body and the centre lead down through 90° about 4mm away. That done, fasten the regulator and its heatsink to the PC board using an M3 × 10mm screw and nut, then solder its leads.

Don't solder the regulator's leads before fastening it down. If you do, you could crack the copper tracks as the mounting screw is tightened.

Trimpots (presets) VR1 to VR6 can now all go in. Be sure to use the correct value in each position.

Note that trimpots are often marked with a value code instead of their ohms value. In this case, the code markings will be 102 for the 1kΩ trimpot (VR1), 201 for the 200Ω trimpot (VR2), 103 for the 10kΩ trimpots (VR3 and VR4) and 503 for the 50kΩ trimpot (VR5).

Mounting the LEDs

LEDs 1 to 17 must all be mounted so that their tops sit exactly 30mm above the PC board. The best way to do this is to cut a 25mm-wide thick cardboard spacer, which can then be slid between the leads of each LED – just push the LED all the way down onto the spacers before soldering its leads.

Take care to ensure that the LEDs are all correctly oriented (the anode (A) lead is the longer of the two) and be sure to use the correct colour 'sleeve' at each location – see Fig.3.

Completing the board

Switch S1, the DC socket (CON1), the LDR and the two sensors can now all be installed. Note that the LDR should be mounted with its top surface about 5mm above the PC board.

The CO sensor (Sensor2) in the red plastic housing can go in either way around. **By contrast, the CO₂ sensor (Sensor1), which is in the metal housing, must be tested for polarity before it is installed. The step-by-step procedure is as follows:**

- 1) Connect short lengths of hook-up wire between each heater pin on the sensor (ie, the centre pin of each set of three pins) and the corresponding pad on the PC board (polarity not important).
- 2) Plug the appropriate DC connector into the plugpack lead, so that the '+' marking on the connector plug aligns with the '+' marking on the connector socket.
- 3) Adjust VR1 fully anticlockwise, then connect a digital multimeter between GND and TP1. Set the meter so that it can measure up to 6V DC.
- 4) Connect the plugpack to the DC socket, switch on and adjust VR1 for a reading of 6V on the DMM. That done, check for +5V on TP6.
- 5) Connect the multimeter to the A and B terminals of the CO₂ sensor. You should get a reading of 300 to 500mV. Identify which terminal is positive and mark it with a '+' sign.
- 6) Switch off, disconnect the heater wiring and mount the CO₂ sensor on the PC board with the positive (+) side oriented as shown on Fig.3.
- 7) Solder the PC stake adjacent to the CO₂ sensor to the sensor's body.


Fitting the microcontroller

You can now fit the microcontroller (IC1) in its socket, taking care with the orientation. That done, apply power again and check that LED17 (the power LED) lights.

If all is well so far, check that this LED dims when the LDR is covered over, and adjust VR6 for best dimming results. (Note: adjustment of the dimming threshold is best done at night.)

Initial adjustments

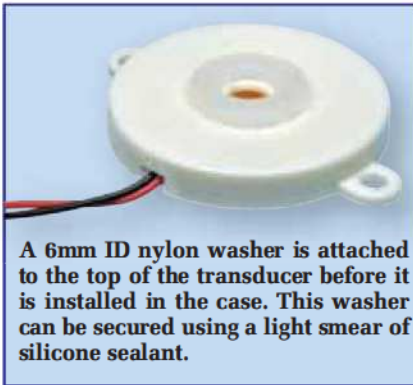Before using the unit, it's necessary to adjust the full-scale sensitivity and threshold level of each 'bargraph'



A 6mm ID nylon washer is attached to the top of the transducer before it is installed in the case. This washer can be secured using a light smear of silicone sealant.

display. The initial procedure is as follows:

- 1) Adjust trimpot VR3 (CO₂ level) to give 3V at test point TP3. This sets the CO₂ full-scale sensitivity to about 10,000ppm or 1%.
- 2) Adjust trimpot VR4 (CO level) to give 3V at TP4. This sets the full-scale CO sensitivity to about 300ppm.

Note: rotating trimpots VR3 and VR4 clockwise will increase the sensitivity of the CO₂ and CO bargraphs respectively (ie, the display will read higher for a given gas concentration). However, do not rotate VR3 for less than 2V at TP3 or VR4 for less than 2V at TP4.


Conversely, rotating each level trimpot anti-clockwise lowers the sensitivity of its corresponding bargraph.

- 3) Adjust VR2 so that the bottom LED of the CO₂ bargraph just extinguishes (ie, no LEDs lit). This should be with test point TP2 at just under 3V.
- 4) Wait 60s after applying power, then blow on the CO₂ sensor to expose it to extra CO₂ gas. Check that the CO₂ bargraph now shows a full-scale reading (ie, top LED lit). If the piezo transducer is connected, check that the alarm sounds with any of the top three LEDs lit.

CO sensor adjustments

Making the adjustments for the CO sensor is a slow process, since it requires a 'burn-in' period of 48 hours. **The unit must, therefore, be left on for 48 hours before making the final adjustments.**

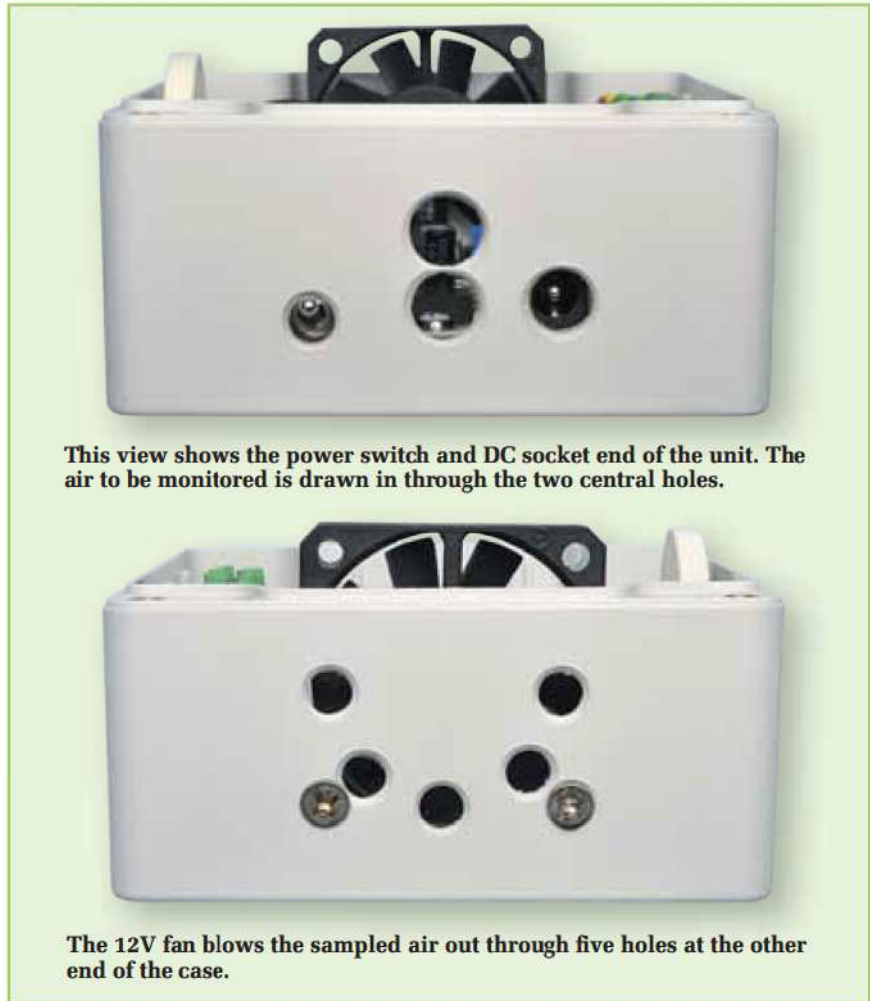Additionally, as stated in the circuit description, the sensor is heated for 60s and then allowed to respond to the gas over a 90s period before each measurement is made. This means that it will take 2.5 minutes to get the result after each adjustment.



This view shows the power switch and DC socket end of the unit. The air to be monitored is drawn in through the two central holes.

The 12V fan blows the sampled air out through five holes at the other end of the case.

Initially, however, you can bypass the 48-hour burn-in period and make the initial adjustments straight away. The final 'touch-up' adjustments can then be made after the burn-in period.

The first step is to adjust trimpot VR5 so that TP5 is at 0.5V right towards the end of the 90s measurement period, ie, when the sensor is in fresh air. However, this requires some means of monitoring the heating and measurement cycles.

In practice, you can either use a second multimeter to monitor the drain (D) of Q5, or use a diagnostic tool that's built into the Air Quality Monitor that shows the heating/measurement cycles.

The procedure for each method is as follows:

METHOD 1: if you have a second multimeter, connect it between Q5's tab (ie, its drain) and GND. Q5's tab will be close to 0V during the heating cycle and at 4.3V during the measurement cycle. Adjust VR5 to set TP5 to 0.5V near the end of the 90s measurement cycle.

METHOD 2: if using the inbuilt diagnostic tool, start by adjusting VR4 fully clockwise, so that TP4 is at 0V. This will now cause the CO bargraph display to show the heating and measurement cycle.

During the 60s heating cycle, the top two red LEDs will be lit. Then, during the 90s measurement cycle, the red LEDs switch off and the four green and two orange LEDs initially light. These LEDs then extinguish one at a time, starting with the topmost orange LED and continuing at 15s intervals until the bottom green LED goes out at the end of the 90s period.

The unit then reverts to the heating mode again, with the top two LEDs lit.

Note that if VR4 is not set all the way down to 0V, only the top LED will light. Additionally, the alarm will sound if VR4 is set below 2V, so the piezo transducer should be unplugged during this procedure.

Assuming VR4 is set for 0V at TP4, it's just a matter of adjusting VR5 so that TP5 is at 0.5V when the lowest

Constructional Project

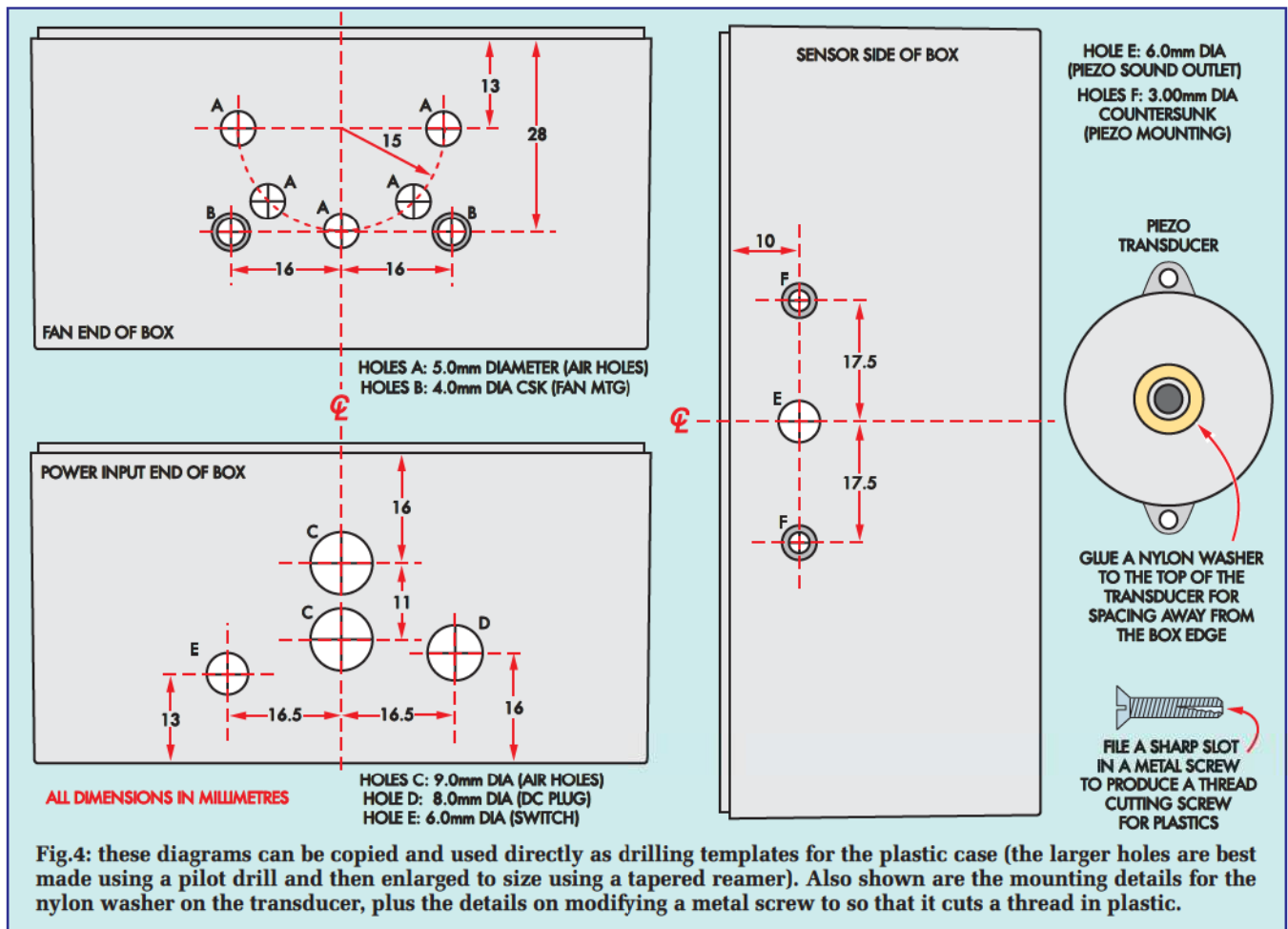


Fig.4: these diagrams can be copied and used directly as drilling templates for the plastic case (the larger holes are best made using a pilot drill and then enlarged to size using a tapered reamer). Also shown are the mounting details for the nylon washer on the transducer, plus the details on modifying a metal screw to so that it cuts a thread in plastic.

one or two green LEDs are alight. Once that's done, be sure to readjust VR4 so that TP4 is at 3V.

Testing the CO sensor

The best way to confirm that the CO sensor is working correctly is to expose it to car exhaust fumes for at least 2.5 minutes.

This can be done by first capturing some exhaust in a length of plastic tubing (eg, 120mm × 16mm-diameter) that's closed at one end. The open end is then held over the CO sensor for 2.5 minutes, during which time the CO bargraph display should rise to full scale.

The display should subsequently switch off again a few minutes after the tube is removed. If it does all this, then the sensor and its circuit are working correctly.

As an aside, it's worth noting that the voltage on TP5 has to rise from the 0.5V fresh-air setting to 2V before the lower LED lights on the CO bargraph. This has been done to prevent the CO bargraph from being oversensitive for readings below 30ppm.

Fitting the board in a case

The PC board is designed to fit inside a standard IP65 ABS box with a clear lid (Jaycar HB-6246 or equivalent). Before installing it though, you need to drill a few holes to mount the fan and the piezo transducer. You also need to drill clearance holes for the on/off switch (S1) and the DC power socket, a hole directly in front of the piezo transducer and, intake and exhaust holes for the fan.

Fig.4 shows the drilling details. It can be copied and cut into sections to make drilling templates.

Once the holes have been drilled, glue a 6mm ID nylon washer to the top of the piezo transducer (using silicone sealant), then tap the two mounting holes in the transducer to 3mm. If you don't have an M3 tap, then a modified M3 metal screw will suffice to cut the thread – see Fig.4.

All you have to do is file a slot along the thread of the screw, with a deeper cut at the thread end. This slot will assist in the cutting and

removal of the plastic to form the thread in each hole.

Similarly, the two bottom mounting holes in the fan housing must be tapped to 4mm. You can use a modified 4mm machine screw (ie, with a slot) to cut the threads if you don't have a proper M4 tap.

The PC board can now be slid into the case and secured using four M3 × 6mm machine screws. That done, secure the fan using two M4 × 12mm countersunk (CSK) head screws, then install the transducer. The latter is fitted with its attached nylon washer against the side of the case and secured using two M3 × 10mm CSK nylon screws (don't over-tighten these screws).

Next, attach the transducer's leads to the 2-way female pin header (the polarity is not important) and plug it into the matching male header on the PC board. The fan can then be wired to the screw terminal block, with the red lead going to the '+' terminal and the black lead to the '-' terminal.

Now check to make sure that the 10 μ F capacitor at the top end of IC1 doesn't foul the fan. It may be necessary to bend the capacitor back towards IC1 slightly, to ensure adequate clearance.

LED tubing

Each LED can be made to project its light onto a small spot on the front panel label by fitting it with a small light guide made from heatshrink tubing – see photos. You will need 17 $\times$ 20mm lengths of 5mm-diameter heatshrink tubing, it's a good idea to use red, yellow and green tubing, so that it matches the colours of the LEDs. Alternatively, you can just use black heatshrink.

Once the heatshrink tubes have been cut to length, slide them down over their respective LEDs by about 6mm and shrink them down by gently applying heat from a hot-air gun. They should each form a tight grip around the LEDs and be left with a small circle at the top.

Finally, adjust the LEDs so that the 'light pipes' are all in a straight line. Now, when the lid is in place, each bargraph LED will project a small spot onto its correct position when it is lit. The same goes for the power LED.

Front panel label

The front panel label can be made by 'scanning' Fig.5 and printing it out on clear overhead projector film. It is then fitted in place inside the clear plastic lid and secured using neutral-cure silicone sealant at each corner.

Installation

The Air Quality Monitor should be mounted near to the combustion heater and preferably on a wall, so that the display can be easily seen. The box has mounting holes that are accessed with the lid off, so it's easy to fix in position.

Note that it's normal for CO₂ levels to rise while the heater is on. However, the ventilation should be increased if the indicated level rises past the low region on the bargraph.

The carbon monoxide (CO) level in the room should be kept to an absolute minimum and this can be achieved by ensuring that the heater is operating correctly. With wood heaters, this means allowing the temperature to rise sufficiently after the fire has been started, to ensure clean combustion,



Fig.5: the full-size front panel artwork.

Below: the completed prototype with the label in position. The 'light pipes' fitted to the LEDs ensure that only the correct 'dots' on the bargraphs are lit.

before reducing the air intake to slow the combustion process.

Finally, never use treated or manufactured timber such as treated pine, medium-density fibreboard (MDF), chip board, hardboard or similar in wood

fires. These products can produce noxious fumes during combustion. **EPE**

Reproduced by arrangement
with SILICON CHIP
magazine 2012.
www.siliconchip.com.au