



ORDER

MY TI

English

日本語

簡體中文

繁體中文

한국어

PRODUCTS

TOOLS

COMPANY

Search For..

Go

Snubber Circuit Design

Home > Power Management > Snubber Circuit Design

Snubber Design Tips

Snubbers are used to limit switching transients and help lower EMI.

1) Measure the ring frequency at the top of the MOSFET switch node (SW) turn-off waveform. Solder a good quality COG or film type capacitor from the MOSFET SW node to GND, causing the ring frequency to be half of the original value. The effective capacitance at this node is 1/3 of the external capacitor value. The stray inductance is calculated using:

$$F_{RING} = \frac{1}{2\pi\sqrt{L_S \times C_T}}$$

where C_T is the total (effective plus external) capacitance.

2) In order to critically damp the ringing, double the size of the external cap. Use a series R calculated from:

$$d = \frac{R}{2} \times \sqrt{\frac{L_S}{C_S}}$$

where d is the damping factor, set to a value of 1. C_S is the calculated effective capacitance at the SW node, **not** the external snubber capacitance.

3) Install the snubber resistor in the ground side of the RC circuit. If the ringing is not critically damped, the external capacitor value is too low. However, increasing this value may not be practical. Measure the positive and negative voltage spikes across the snubber resistor, which will be highest at the maximum input voltage. The power dissipated in the resistor is calculated by:

$$P(R_{SNUB}) = \frac{1}{2} \times C_{SNUB} \times (V_P^2 + V_N^2) \times F_{SW}$$

where V_P and V_N represent the positive and negative voltage spikes across the snubber resistor, and F_{SW} is the switching frequency.

This could be an unacceptably high amount of power dissipation. If so, a compromise between efficiency and damping may be required.

For parallel damping, the relationship is:

$$d = \frac{1}{2R} \times \sqrt{\frac{L_S}{C_S}}$$

or

$$R_{SNUB} = \frac{1}{2d} \times \sqrt{\frac{L_S}{C_S}}$$


For critical damping ($d = 1$):

For critical damping ($d = 1$):

$$C_{\text{SNUB}} \geq 5 \times C_S$$

$$R_{\text{SNUB}} = \frac{1}{2} \times \sqrt{\frac{L_S}{C_S}}$$

 Buck Regulator Snubber Circuit Design Example



Measure the switching signal at the MOSFET/inductor junction. You will see a voltage spike and ringing at the top of this signal. Let's say you measure a ring period of 7 ns, which represents 143 MHz. Solder a capacitor directly across the low side FET from the switch node to ground. Let's say 330 pF causes the period to double to 14 ns.

Calculate C_S from:

$$C_S = C_{\text{EXT}} / 3 = 330 \text{ pF} / 3 = 110 \text{ pF}$$

Calculate L_S from:

$$L_S = \frac{1}{C_S \times (2\pi \times F_{\text{RING}})^2} = \frac{1}{110 \text{ pF} \times (6.28 \times 143 \text{ MHz})^2} = 11.2 \text{ nH}$$

Calculate C_{SNUB} from:

$$C_{\text{SNUB}} \geq 5 \times C_S$$

$$C_{\text{SNUB}} \geq 5 \times 110 \text{ pF} = 550 \text{ pF} ; \text{ use } 560 \text{ pF}$$

Calculate R_{SNUB} from:

$$R_{\text{SNUB}} = \frac{1}{2} \times \sqrt{\frac{L_S}{C_S}} = \frac{1}{2} \times \sqrt{\frac{11.2 \text{ nH}}{110 \text{ pF}}} = 5 \text{ ohms}$$

Install R_{SNUB} and C_{SNUB} .

Lets say at 40V input you measure $V_{\text{pos}} = 40\text{V}$ and $V_{\text{neg}} = 20\text{V}$ across the resistor.

For 150 kHz operation:

$$P(R_{\text{SNUB}}) = \frac{1}{2} \times C_{\text{SNUB}} \times (V_P^2 + V_N^2) \times F_{\text{SW}} = \frac{1}{2} \times 560 \text{ pF} \times (1600 + 400) \times 150 \text{ kHz} = 0.084 \text{ watts}$$

Learn More Power Supply Design Techniques at:

- [Analog University](#)



For technical questions regarding TI and National Semiconductor products:

- [TI E2E™ Community](#) (engineer-to-engineer online forums where you can ask questions to your fellow engineers and TI experts, as well as search for similar questions/answers)
- [TI Product Information Center](#) (TI's email/phone support hotline for your region of the world)

[Site Map](#) | [About "Cookies"](#) | [National is ISO/TS16949 Certified](#) | [Privacy/Security Statement](#) | [Contact Us/Feedback](#) | [RSS Feed](#) | [Site Terms & Conditions of Use](#)

Copyright © 2011 National Semiconductor Corporation